



**Fundusze Europejskie**  
Wiedza Edukacja Rozwój



**Rzeczpospolita  
Polska**

**Unia Europejska**  
Europejski Fundusz Społeczny



**Politechnika Śląska jako Centrum Nowoczesnego Kształcenia  
opartego o badania i innowacje**

**POWR.03.05.00-IP.08-00-PZ1/17**

**Projekt współfinansowany przez Unię Europejską ze środków Europejskiego Funduszu Społecznego**

# **Digital Circuits Design**

**Faculty of Automatic Control, Electronics and Computer Science,  
Informatics, Bachelor Degree**

# Lecture 14.

---

## Hardware Description Language - simulation

# Verilog

---

## Contents

- Synthesizable constructions - continuation
- Simulation

# Procedural assignment – always

---

- `always`
  - Each procedural block is executed concurrently
  - Procedural block is endless loop
  - Synthesis is performed with restrictions
  - Enables description of combinational and sequential circuits
  - `always` blocks cannot be nested

- **Event control:** `@ (<sensitivity_list>)`
  - Any change of signal from the sensitivity list results in „an execution” of the always block

```
@ (CLK) Q = D;
```

```
@ (posedge CLK) Q = D; //0->1, x->1, 0->x
```

```
@ (negedge CLK) Q = D; //1->0, x->0, 1->x
```

# Procedural assignment – always

---

- Example 1

```
always @(posedge CLK or negedge CLR)
begin //block; { and } are preserved for concatenation
    if(!CLR)
        Q <= 1'b0;
    else
        Q <= D;
end
```

- Example 2

```
always @(a or b or sel)
    if(sel)
        y = a;
    else
        y = b;
```

# Procedural assignment – always

---

- **Example 1**

```
always @(posedge CLK or negedge CLR)
begin
    if(!CLR) //..... reset
        Q <= 1'b0;
    else
        Q <= D;
end
```

- **Example 3**

```
always @(posedge CLK)
    if(!CLR) //..... reset
        Q <= 1'b0;
    else
        Q <= D;
```

# Procedural assignment

---

- Blocking assignment (=)
  - The expression is evaluated and then assigned to the variable immediately, before execution of the next statement (so „block“ the execution of other statements)
- Nonblocking (<=)
  - Expressions are executed concurrently
  - The order does not matter
  - The expression does not „block“ the execution of statements in another procedural blocks
- Do not mix blocking and nonblocking assignments
- Use **blocking** assignments for a **combinational** circuit
- Use **nonblocking** assignments for a **sequential** circuit

# Procedural assignment

---

- Blocking (=)

```
always @(posedge CLK)
begin
  if (CLR)
    begin
      Q1 = 4'b0;
      Q2 = 4'b0;
    end
  else
    begin
      Q1 = IN1; //Q2 = Q1;
      Q2 = Q1; //Q1 = IN1;
    end
end
```

- The order matters!!!

- Nonblocking (<=)

```
always @(posedge CLK)
begin
  if (CLR)
    begin
      Q1 <= 4'b0;
      Q2 <= 4'b0;
    end
  else
    begin
      Q1 <= IN1; //Q2 <= Q1;
      Q2 <= Q1; //Q1 <= IN1;
    end
end
```

- The order does not matter!!!



# Procedural assignment

---

- **Blocking (=)**

```
always @(posedge CLK or posedge rst)
    if(rst)
        Q1 = 1'b0;
    else
        Q1 = Q2;
always @(posedge CLK or posedge rst)
    if(rst)
        Q2 = 1'b1;
    else
        Q2 = Q1;
```

– **Race condition!!!**

- **Nonblocking (<=)**

```
always @(posedge CLK or posedge rst)
    if(rst)
        Q1 <= 1'b0;
    else
        Q1 <= Q2;
always @(posedge CLK or posedge rst)
    if(rst)
        Q2 <= 1'b1;
    else
        Q2 <= Q1;
```

# if-else

---

- `if (<condition>) instr_true;`  
`[else instr_false;]`
- `if-else` can be nested
- Use `if-else` for combinational logic  
`else` is not necessary for sequential logic

- **Example**

```
if(EN) Q = A;
```

```
if(Q < MAX) Q = Q + 1;
```

```
else Q = 0;
```

```
if(CTRL == 0)
```

```
    S = A + B;
```

```
else if(CTRL == 1)
```

```
    S = A - B;
```

```
else if(CTRL == 2)
```

```
    S = A * B;
```


```
else S = A;
```

# Implicated „latch”

```
module impl_latch(a, enable);
input [1:0] a;
output reg enable;

always @(a)
  if(a<1)
    enable=1'b1;
  else
    if(a>2)
      enable=1'b0;

endmodule
```

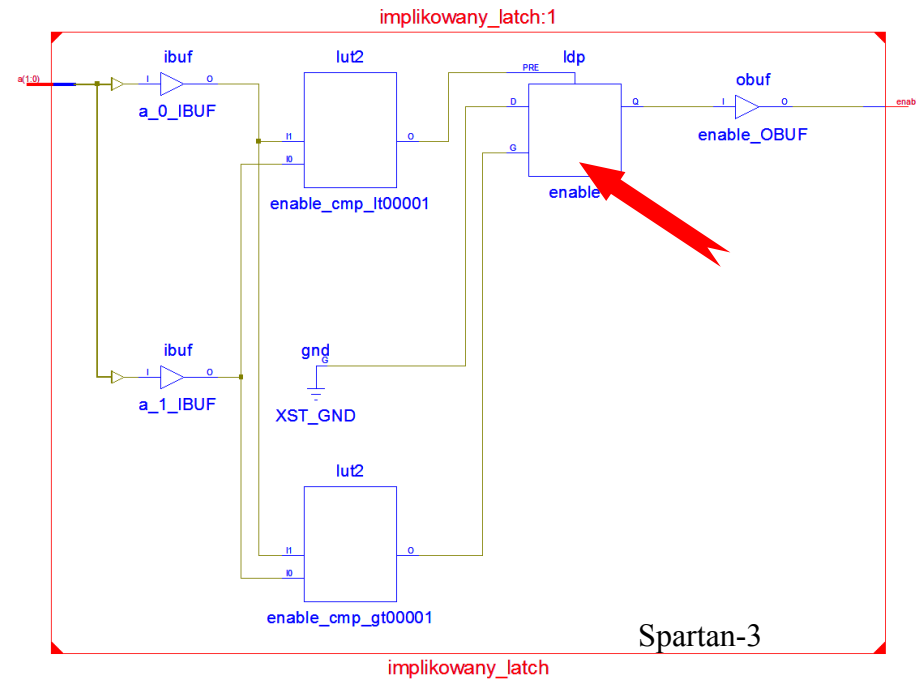

## ◆ Other examples

```
if(a>10)
  enable=1'b1;
```

```
if(a>10)
  enable=1'b1;
else
  driver=1'b0
```

```
always @(in_a or in_b or sel)
begin
  case (sel)
    2'b00: out_a = in_a;
    2'b01: out_a = in_b;
  endcase
end
```

# case

---

- Enables comparison the `expression` with `item` expressions and execute particular statement/statements

```
case (<expression>)  
  item_1: instr_1;  
  ...  
  item_n: instr_n;  
  default: instr_def;  
endcase
```

- **Example**

```
case (CTRL)  
  2'd0: S = A + B;  
  2'd1: S = A - B;  
  2'd2: S = A * B;  
  default: S = A;  
endcase
```

# for loop

---

- `for (<e>, <c>, <i>)` is consisted of:
  - `<e>` initialization
  - `<c>` condition
  - `<i>` increment/decrement

- **Example**

```
parameter w = 8;
input [w-1:0] D;
reg [w-1:0] Q;
integer i;

always @(posedge CLK)
begin
    for(i=0; i<w; i=i+1)
        Q[i] <= D[i];
end
```

# for loop

---

- rd84 Example

```
input [7:0] D;
reg [3:0] Y;
integer i, cnt;

always @(posedge clk)
begin
    cnt= 0;
    for(i=0; i<8; i=i+1)
        if(D[i])
            cnt= cnt +1;
    y<= cnt;
end
```

# Verilog

---

- The HDL is a description of the operation and/or **construction** of the electronic circuit
- The source is called a **description** or **model**
- **Designed to simulate**

# Module/instance – simulation

---

```
module COUNTER(Q,CLK,CLR);  
input CLK,CLR;  
output [2:0] Q;  
  
//instances of the TFF module  
TFF tff0(Q[0],CLK ,CLR);  
TFF tff1(Q[1],Q[0],CLR);  
TFF tff2(Q[2],Q[1],CLR);  
  
endmodule
```

```
module TFF(...  
...  
endmodule
```





# Procedural blocks – `always` and `initial`

---

- Every procedural block is „executed” concurrently
- Simulation of every block begins in so called zero simulation time
- `initial` and `always` cannot be nested

# `always` block in simulation

---

- „Execution” (simulation) of the procedural block begins at 0 time
- Block is „executed” as endless loop
- Initialization of signals from `always` block must be performed by using `initial` block
- Define the end of simulation because `always` is endless loop - otherwise the simulation will not end!

# Initial block

---

- „Execution” of the procedural block begins at 0 time
- `initial` block is „executed” once during simulation
- It is not synthesizable!

```
module BEHAV;  
reg CLK;  
  
initial  
begin  
    CLK = 1'b0;  
    forever #5 CLK = ~CLK;  
end  
  
initial  
    $monitor("%t: CLK: %b", $time, CLK);  
endmodule
```

# Delays

---

```
initial  
begin  
    b = 1'b0;  
    #10 a = b;  
    //wait 10 time units; take b and assign to a  
end
```

```
initial  
begin  
    x = 1'b0; y = 1'b1;  
    z = #10 x + y;  
    //count x + y; wait 10 time units; assign to z  
end
```

# Instances and simulation

---

```
module Test;
reg CLK,CLR;
wire [3:0] Q;

CNT C1(Q,CLK ,CLR);

//Clock generator
initial
begin
    //initial value
    CLK = 1'b0;
    //generator
    forever
        #5 CLK = ~CLK;
end
...
```


# Instances and simulation

---

```
//CLR control  
initial  
begin  
    CLR = 1'b1;           //initial value t = 0 CLR = 1  
    #15  CLR = 1'b0;     // t = t + 15 = 15, CLR = 0  
    #180 CLR = 1'b1;     // t = t + 180 = 195, CLR = 1  
    #10  CLR = 1'b0;  
    #20  $finish;       //the end  
end  
  
//monitor function  
initial  
    $monitor("%t: %b %b : %d", $time, CLK, CLR, Q);  
  
endmodule
```

# Simulation

- Stimulation test

 

- \$monitor

0:	0	1	:	0
5:	1	1	:	0
10:	0	1	:	0
15:	1	0	:	1
20:	0	0	:	1
25:	1	0	:	2
30:	0	0	:	2
35:	1	0	:	3
40:	0	0	:	3
45:	1	0	:	4
50:	0	0	:	4
55:	1	0	:	5

60:	0	0	:	5
65:	1	0	:	6
70:	0	0	:	6
75:	1	0	:	7
80:	0	0	:	7
85:	1	0	:	8
90:	0	0	:	8
95:	1	0	:	9
100:	0	0	:	9
105:	1	0	:	10
110:	0	0	:	10
115:	1	0	:	11



# Structural procedures

---

```
module stimulus;
reg a, b;

initial
    b = 1'b0;

initial begin
    #10 a = 1'b0;
    #15 a = 1'b1;
    #5  b = 1'b1;
end

initial
    #50 $finish;

endmodule
```

```
module CLKGEN;
reg clock;
parameter hper = 10;

initial
    clock = 1'b0;

always
    #hper clock = ~clock;

initial
    #1000 $finish;


endmodule
```

# Procedural assignment

---

Blocking (=)

 
```
initial
begin
  b = 1'b0;
  #10 a = 1'b0;
  #15 a = 1'b1;
  #5  b = 1'b1;
end
```



time	Event
0	b = 0
10	a = 0
25	a = 1
30	b = 1

Nonblocking (<=)
 
```
initial
begin
  b = 1'b0;
  a <= #10 1'b0;
  a <= #15 1'b1;
  b <= #5 1'b1;
end
```



Time	Event
0	b = 0
5	b = 1
10	a = 0
15	a = 1

# Directives

---

- Time

```
`timescale <ref_time_unit>/<time_precision>
```

```
`timescale 1ns / 1ps
```

---

Based on:

Robert Czerwiński „Digital Circuits Design” lecture