



Fundusze
Europejskie
Wiedza Edukacja Rozwój



Rzeczpospolita
Polska

Unia Europejska
Europejski Fundusz Społeczny



**Politechnika Śląska jako Centrum Nowoczesnego Kształcenia
opartego o badania i innowacje**

POWR.03.05.00-IP.08-00-PZ1/17

Projekt współfinansowany przez Unię Europejską ze środków Europejskiego Funduszu Społecznego

Digital Circuits Design

**Faculty of Automatic Control, Electronics and Computer Science,
Informatics, Bachelor Degree**

Lecture 8.

SEMICONDUCTOR MEMORY



Ph.D. Eng. Adam Opara


Memory

Agenda:

- Introduction
- Parameters and signals
- Semiconductor memory classification
 - Read Only (ROM, PROM)
 - Non volatile (EPROM, EEPROM, NVRAM, FLASH EEPROM, FRAM, MRAM)
 - Volatile
 - RAM (SRAM, DRAM – EDO, SDRAM , DDR, VSRAM)
 - Special (FIFO, LIFO, associative CAM, dual port)
- Organizing memory blocks

Memory

 - Devices used to store a digital information
(analog devices also exist!)
 - Operational (data and prog. used by μ P - semiconductor)
 - External (eg. HDD)



Memory


- Parameters
 - Capacity - # of cells
 - Word length (organization #words x #word length)
 - Access time
 - Memory cycle (+ regeneration)
 - Power per bit (technology: bipolar, CMOS)

Memory

- Signals
 - Address (input)
 - Data (input)
 - Data (output)
 - Control
 - Chip enable or chip select \overline{CE} , \overline{CS}
 - Access type \overline{OE} , \overline{WE} , R/ \overline{W}
 - Enable programming (non-volatile mem.)

Memory parameters

 - Read timing. The access time measured from change of
 - address t_{AA}
 - chip enable t_{ACE}
 - read signal t_{ARD}




t_{HD1} - hold data time after decaying A

t_{HD2} - hold data time after decaying CE

Memory parameters

- Write timing.

 

t_{AS} – address setup

t_{AH} – address hold

t_{CSW} – chip select before write

t_{WP} – write pulse minimum width


t_{DS} – data setup

t_{DH} – data hold

ROM

- Read Only Memory

Programmed during manufacturing

 


ROM

- Read Only Memory

Programmed during manufacturing

Application:

 - character generator,
- code converter,
- multiplier,
- μ P program
- A/D, D/A nonlinearity correction
- combinatorial circuits



PROM


- Programmable ROM

mostly bipolar

10ns-50ns

<128Kb

One time user programmable

 


EPROM

- Erasable PROM



Programming:

 - high U \rightarrow c. gate
- electrons \rightarrow f. gate






Erasing:

  - quartz glass window
- UV 2537 A, $15\text{Ws}/\text{cm}^2$,
15...30 min.




EEPROM

- Electrically Erasable PROM

   

EEPROM programming

 


Mode	CE	OE	WE	D	BUSY
Read	0	0	1	D _{OUT}	HiZ
Idle	1	-	-	HiZ	HiZ
Write	0	1	0	D _{IN}	0

NVRAM

- Battery-backed SRAM
- EEPROM+SRAM in parallel
 - Fast
 - Non Volatile

	\overline{CE}	\overline{OE}	\overline{WE}	\overline{NE}
read	0	0	1	0
write	0	1	0	0
recall	0	0	1	1
store	0	1	0	1

$< 10\mu s$ $10ms$

 

FLASH

- Fast erase (sector/block)
 - Programming wr 0 like in EPROM
-
- NAND FLASH – high density
 - NOR – high durability

New NV memories


- Ferroelectric RAM (FRAM)
 - Programmable capacitors, dielectric crystals polarize under electric field
 - High density, many RD/WR
 - Low power
- Magnetoresistive RAM (MRAM)
 - Like magnetic core memory
 - Spin electron or tunneling magnetic resistance

SRAM


Static RAM

- Fast
- 1 cell = 1 flip flop (4-6 transistors)
- High power dissipation


SRAM

 


SRAM – memory cell

 

SRAM – memory cell

 

NVRAM – EEPROM+SRAM

 


DRAM

Dynamic RAM


- Slower than Static RAM
- 1 cell = 1 transistor + capacitance
- Refresh

DRAM

 


DRAM

Memory cell

 


DRAM

Read

 


Write

 


DRAM

 Std. CAS writes column addr. and enables output




 Static columns change of addr. automatically detected, no CAS sync.




DRAM


Nibble/EDO fast access to 4 data cells

 

 FastPage/EDO fast access to a few columns




Pipelined Burst EDO Nibble+FastPage

 


DRAM – refresh timing


RAS only refresh

 

CAS before RAS (internal counter)

 


 Hidden (additional RAS during read cycle)




SDRAM

Asynchronous DRAM

 

Synchronous DRAM

 

Double Data Rate DDR DRAM




DDR - speed

Name		Release	Chip	Bus		Voltage
Generation	Standard	year	Clock rate	Clock rate	Bandwidth	[V]
			[MHz]	[MHz]	[MB/s]	
DDR	DDR-200	2000	100 (10ns)	100	1600	2.5
	...					
	DDR-400		200	200	3200	2.6
DDR2	DDR2-1066	2003	266 $\frac{2}{3}$	533 $\frac{1}{3}$	8533 $\frac{2}{3}$	1.8
DDR3	DDR3-2133	2007	266 $\frac{2}{3}$	1066 $\frac{2}{3}$	17066 $\frac{2}{3}$	1.5/1.35
DDR4	DDR4-3200	2014	400 (2,5ns)	1600	25600	1.2/1.05
DDR5		2020				


DRAM - Row hammer

- Row hammer attack - without exploiting software bugs
 - Y. Kim; R. Daly; J. Kim; C. Fallin; J.H. Lee; D. Lee; C. Wilkerson; K. Lai; O. Mutlu (June 24, 2014). "*Flipping Bits in Memory Without Accessing Them: An Experimental Study of DRAM Disturbance Errors*". ece.cmu.edu. IEEE. Retrieved March 10, 2015.

DDR - Row hammer

 

DDR - Row hammer

 

DDR - Row hammer

- How we can defend?
 - ECC error correction
 - Refreshing neighbors

Memory

- Organizing memory blocks
 - data width
 - address width