



Fundusze  
Europejskie  
Wiedza Edukacja Rozwój



Rzeczpospolita  
Polska

Unia Europejska  
Europejski Fundusz Społeczny



**Politechnika Śląska jako Centrum Nowoczesnego Kształcenia  
opartego o badania i innowacje**

**POWR.03.05.00-IP.08-00-PZ1/17**

Projekt współfinansowany przez Unię Europejską ze środków Europejskiego Funduszu Społecznego

# **Digital Circuits Design**

**Faculty of Automatic Control, Electronics and Computer Science,  
Informatics, Bachelor Degree**

# Lecture 1

---

## Digital IC Parameters – part 1

Bartłomiej Zieliński, PhD, DSc

# Parameters – part 1

---

Program:

(today)

- Parameter groups
- Functional parameters
- Dynamic parameters

(next week)

- Static parameters
- Operational conditions parameters
- Clock asynchronism, example values

# Parameters – part 1

---

- Properties of digital IC are described by external parameters
  - Proper choice of IC
  - Optimal properties utilisation
- Digital IC's production
  - Large series, constant proces
  - Various applications
  - Various conditions
- Full exchangeability rule
  - An IC can be replaced with another one of the same type without influence on device operation
  - No preselection of IC's is necessary

# Parameters – part 1


---

- Parameter groups
  - Functional parameters
    - Describe functional IC properties
  - Dynamic parameters
    - Time dependencies
  - Static parameters
    - Voltage levels, current values, cooperation conditions
  - Parameters describing IC operating conditions
    - E.g., power supply, temperature, humidity, etc.
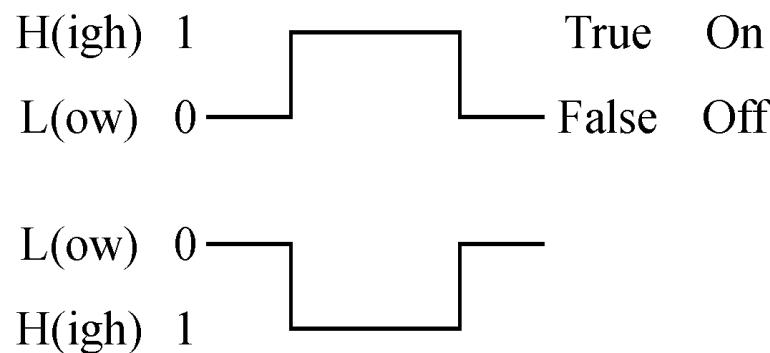
# Parameters – part 1

---

- Functional parameters
  - Logic, arithmetic function of IC
  - Logic convention must be accepted first
    - Positive convention – most of digital IC's
      - TTL
      - CMOS
    - Negative convention
      - RS-232
      - ECL



# Parameters – part 1

- Inputs influence on each other and on the circuit

- Inputs:







- Information (data to be processed; syn/asyn)
    - Control (function to be performend; syn/asyn)
    - Synchronisation (clock)

- Signal synchronism

- Asynchronous – signal influences all the time it's active
    - Synchronous – signal influences only at the moments specified by clock

- Device synchronism

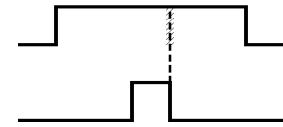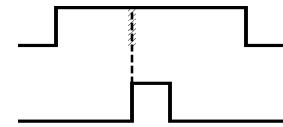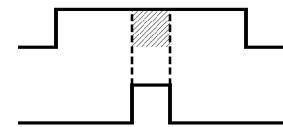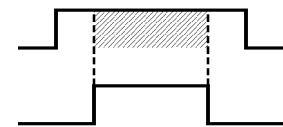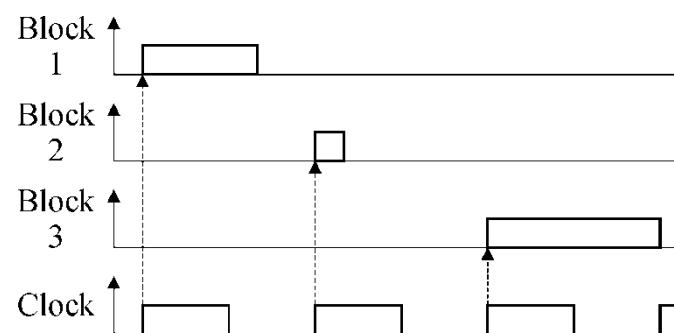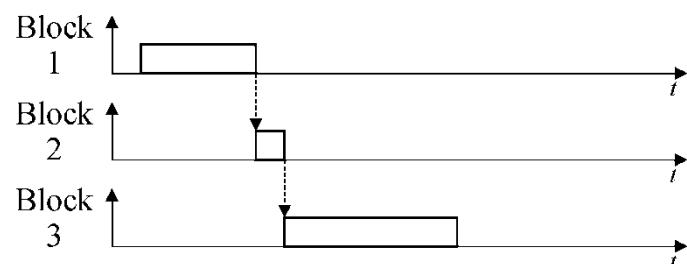- Asynchronous – once a block finishes its task, the next one can start immediately
    - Synchronous – the next block can start a task only at the moment specified by clock



# Parameters – part 1

- Inputs influence on the circuit

- Level sensitive
- Edge/sequence of edges sensitive




- Input/output marking on the diagram



- Gates and other elements symbols

- Few different standards

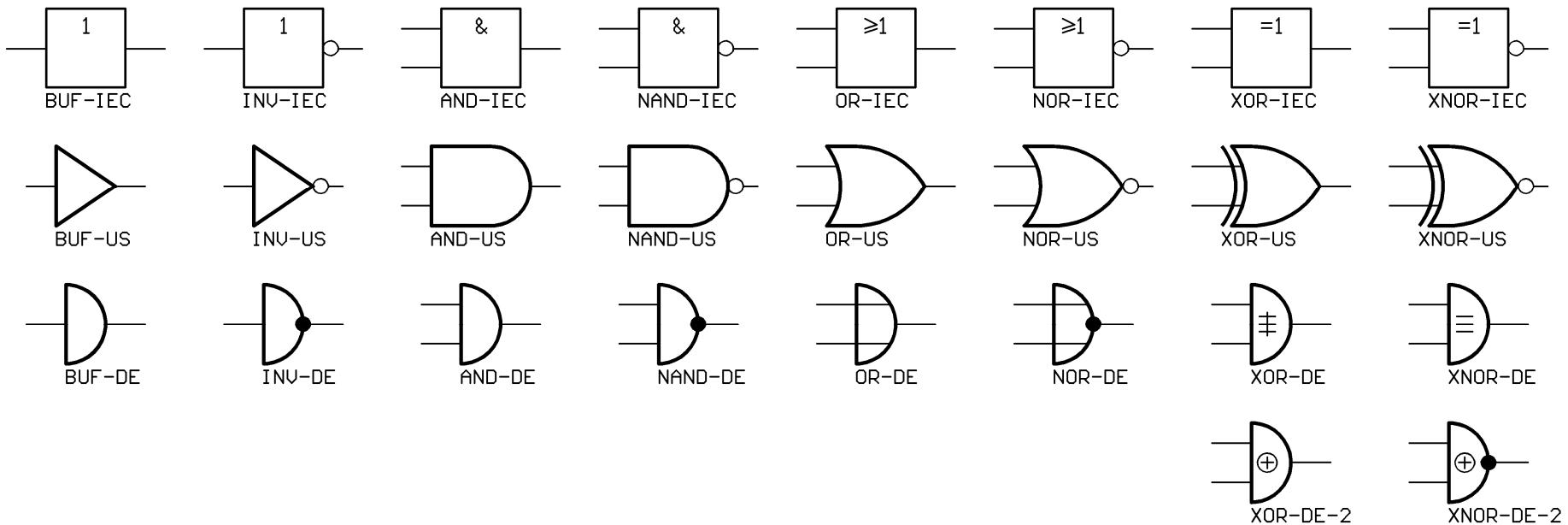

# Parameters – part 1

---

- Gates and other elements symbols


Logic function	American (MIL/ANSI) Symbol	British (BS3939) Symbol	Common German Symbol	International Electrotechnical Commission (IEC) Symbol
Buffer	IN OUT 	IN OUT 	IN OUT 	IN OUT 
Inverter (NOT gate)	IN OUT 	IN OUT 	IN OUT 	IN OUT 
2-input AND gate	IN OUT 	IN OUT 	IN OUT 	IN OUT 
2-input NAND gate	IN OUT 	IN OUT 	IN OUT 	IN OUT 
2-input OR gate	IN OUT 	IN OUT 	IN OUT 	IN OUT 
2-input NOR gate	IN OUT 	IN OUT 	IN OUT 	IN OUT 
2-input EX-OR gate	IN OUT 	IN OUT 	IN OUT 	IN OUT 
2-input EX-NOR gate	IN OUT 	IN OUT 	IN OUT 	IN OUT 

# Parameters – part 1

---

- Unit load:

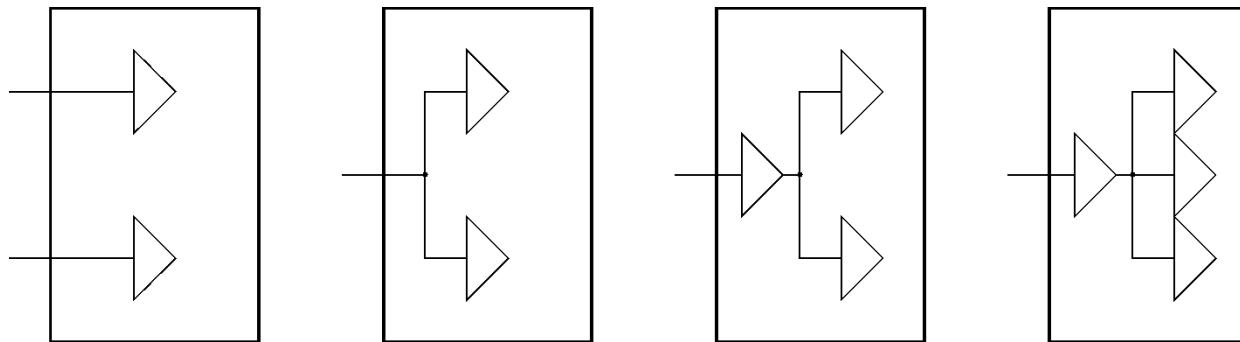- Load caused by a single input of a standard logic gate in a given technology
- Makes sense only if all the elements belong to the same family
- If an input controls more internal signals, the load is a multiple of the unit load




- Outputs

- Load (logic gain) – number of inputs of IC belonging to the given family, that can be driven by the output without exceeding/violating its parameters
- Typical logic gain = few to over a dozen
- Output types
- Possibility of output connecting


# Parameters – part 1

---


- Inputs and outputs

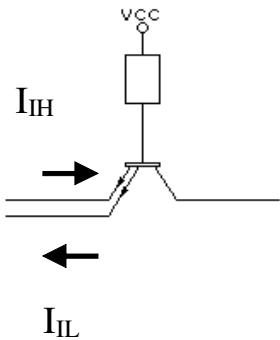


input

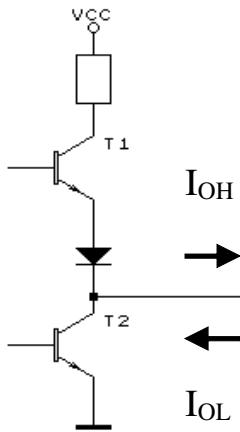

totem-pole output

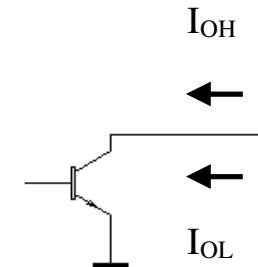


open-collector output

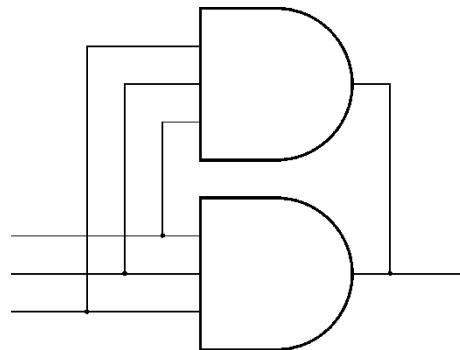

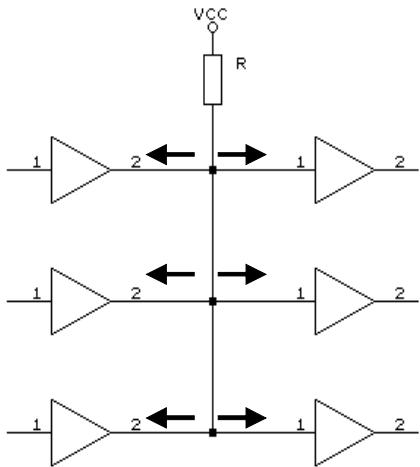
# Parameters – part 1

- Resistor value calculation for open-collector outputs



High state

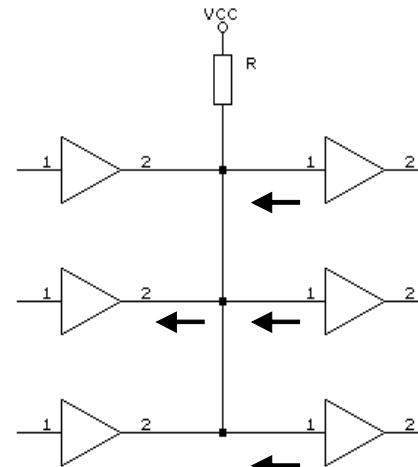

Low state

$$R_{max} = \frac{V_{CC} - \max(U_{OHmin}, U_{IHmin})}{\sum I_{OHmax} + \sum I_{IHmax}}.$$

$$R_{min} = \frac{V_{CC} - \min(U_{OLmax})}{\min(I_{OLmax}) - \sum I_{ILmax}}.$$

# Parameters – part 1


---

- Dynamic parameters
  - Dependencies between input and output signals
    - Corresponding to inputs → determine input driving conditions
    - Relations between inputs and outputs → determine circuit switching speed
  - Non-uniform production, various operating conditions → value ranges rather than exact values
  - Often only min, max and typical (e.g., average) values are given
  - „time rise“ ( $t_r$ ) and „time fall“ ( $t_f$ ) measured between:
    - 10% and 90% of amplitude
    - 20% and 80% of amplitude
    - Some constant  $U_a$  and  $U_b$
  - Time between two edges measure between:
    - 50% to 50% of amplitude
    - Some constant  $U_c$
    - Switching threshold voltage

# Parameters – part 1

---


- An illustration of dynamic parameters

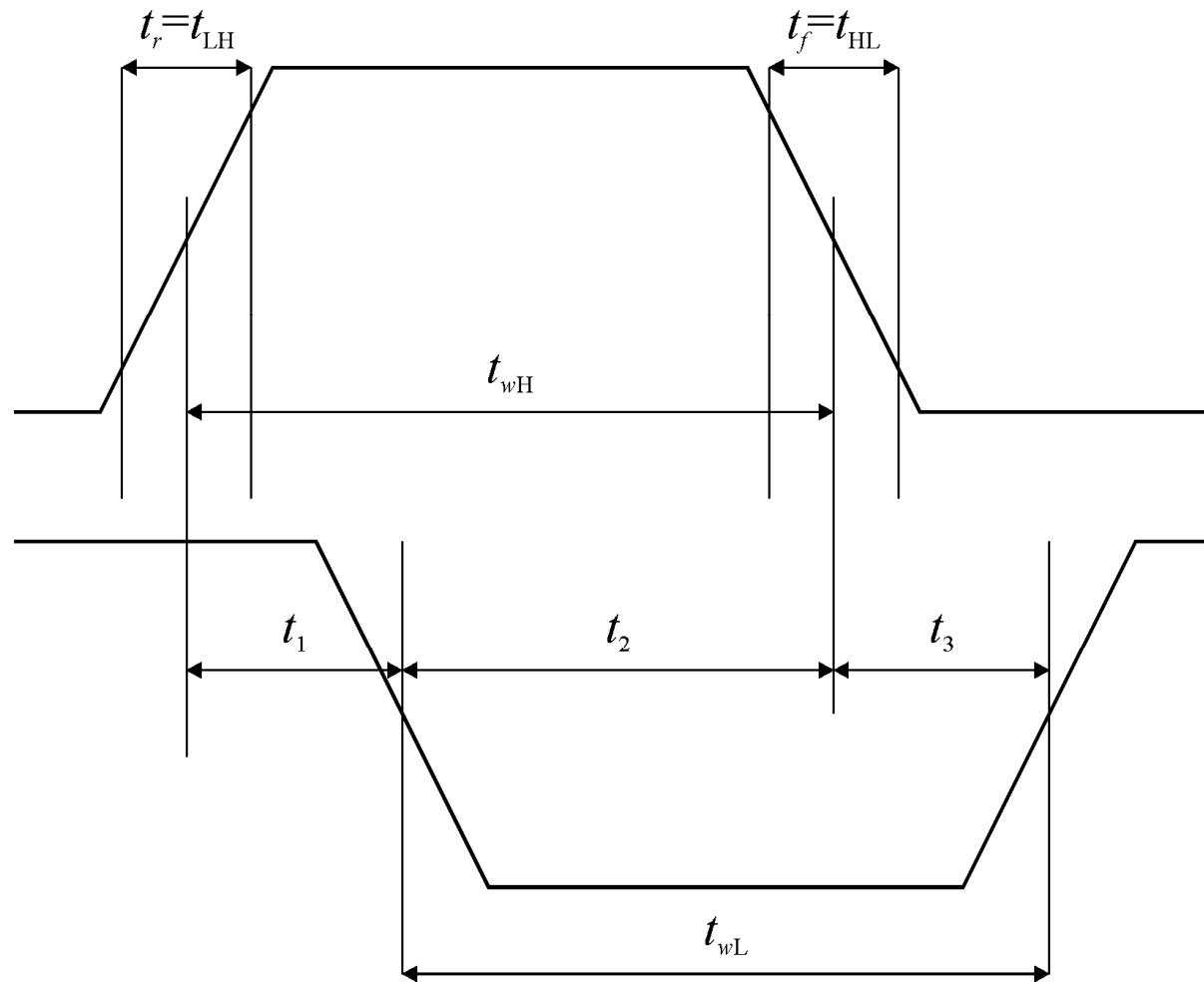
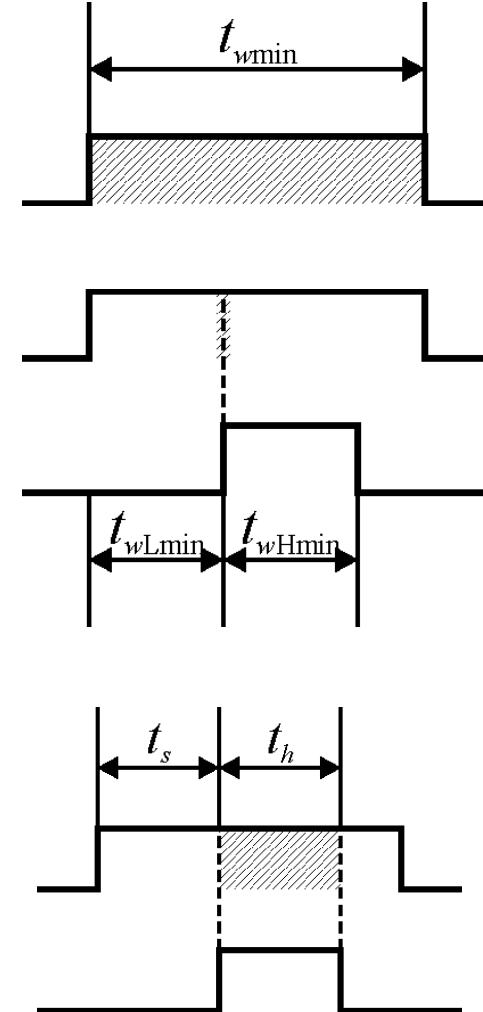
# Parameters – part 1

---


- About dynamic parameters
  - Syn/asyn level sensitive input
    - $t_{w\min}$
  - Edge synchronising input
    - $t_{wL\min}$  (before edge),
    - $t_{wH\min}$  (after edge),
    - $t_{r\max}, t_{f\max}$  (max edge duration)
  - Synchronous level sensitive input  $\rightarrow t_s$  („time set”),  $t_h$  („time hold”)
  - Synchronisation input (clock)  $\rightarrow f_{\max}$  (*de facto* minimal frequency guaranteed)


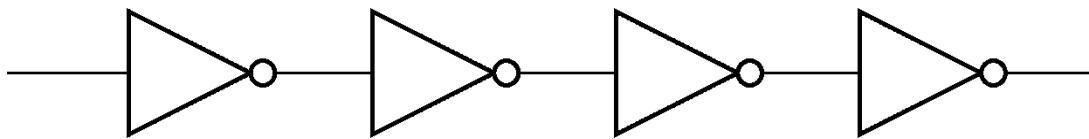
# Parameters – part 1

---

- Propagation time – from input signal change to the effect visible at the output signal
  - Usually only max value → guaranteed not to be exceeded
  - sometimes typical value → the value we can hope for (not guaranteed)
  - Very rarely min value → not necessary for digital system design (except some really special cases...)



$$\Delta t \in \left\langle \sum t_{p_{min}} \dots \sum t_{p_{max}} \right\rangle$$