



Fundusze  
Europejskie  
Wiedza Edukacja Rozwój



Rzeczpospolita  
Polska

Unia Europejska  
Europejski Fundusz Społeczny



**Politechnika Śląska jako Centrum Nowoczesnego Kształcenia  
opartego o badania i innowacje**

**POWR.03.05.00-IP.08-00-PZ1/17**

Projekt współfinansowany przez Unię Europejską ze środków Europejskiego Funduszu Społecznego

# **Digital Circuits Design**

**Faculty of Automatic Control, Electronics and Computer Science,  
Informatics, Bachelor Degree**

# Lecture 4

---

**Time dependencies circuits – part 2**

**Bartłomiej Zieliński, PhD, DSc**

# Time circuits – part 2

---

Program:

(last week)

- 7412x circuit family
- Properties, applications


(today)

- 555 circuit
- CMOS 4000B-family timers
- Differential (trigger) circuits
- Square wave generators
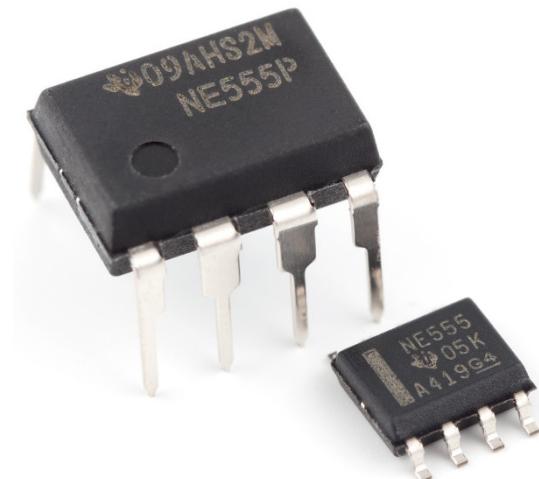
# Time circuits – part 2

---

- 555 circuit
  - NE555
    - Designed in 1971 by Signetics
    - „probably the most popular integrated circuit ever made”
    - DIP8 package
  - NE556
    - 2×NE555 in DIP14 package
  - NE558
    - 4×(not fully independent)NE555 in DIP16 package



# Time circuits – part 2

---

- 555 circuit
  - NE555, UL7855, MC1455, ICM755, TLC555


	Bipolar	CMOS	CMOS
$f_{max}$	100 kHz	500 kHz	1 MHz
$V_{CC}$	5-18 V	2-18 V	1.5-18 V

- Pulse length 5μs...few minutes
- $t_r, t_f < 100 \text{ ns}$
- $I_O \leq 200 \text{ mA}, I_I \leq 1 \mu\text{A}$
- $I_{OL} < 8 \text{ mA} \rightarrow U_{OL} < 0.1 \text{ V}$
- $I_{OH} < 16 \text{ mA} \rightarrow U_{OH} = \text{about } V_{CC} - 1.4 \text{ V}$

# Time circuits – part 2

---

- NE555

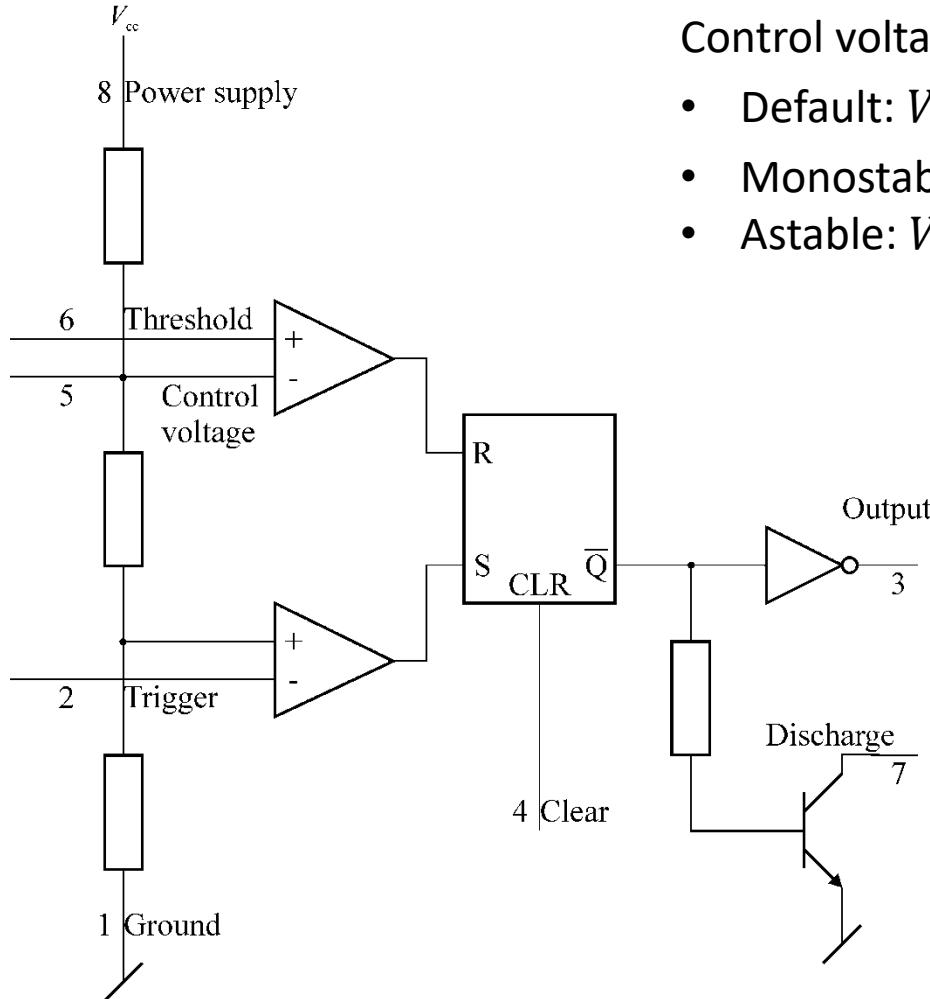


Control voltage

- Default:  $V_5 = \frac{2}{3} V_{CC}$
- Monostable:  $V_5 = 45 \div 90\% V_{CC}$
- Astable:  $V_5 = 1.7V \div V_{CC}$

# Time circuits – part 2

- NE555 as a monovibrator

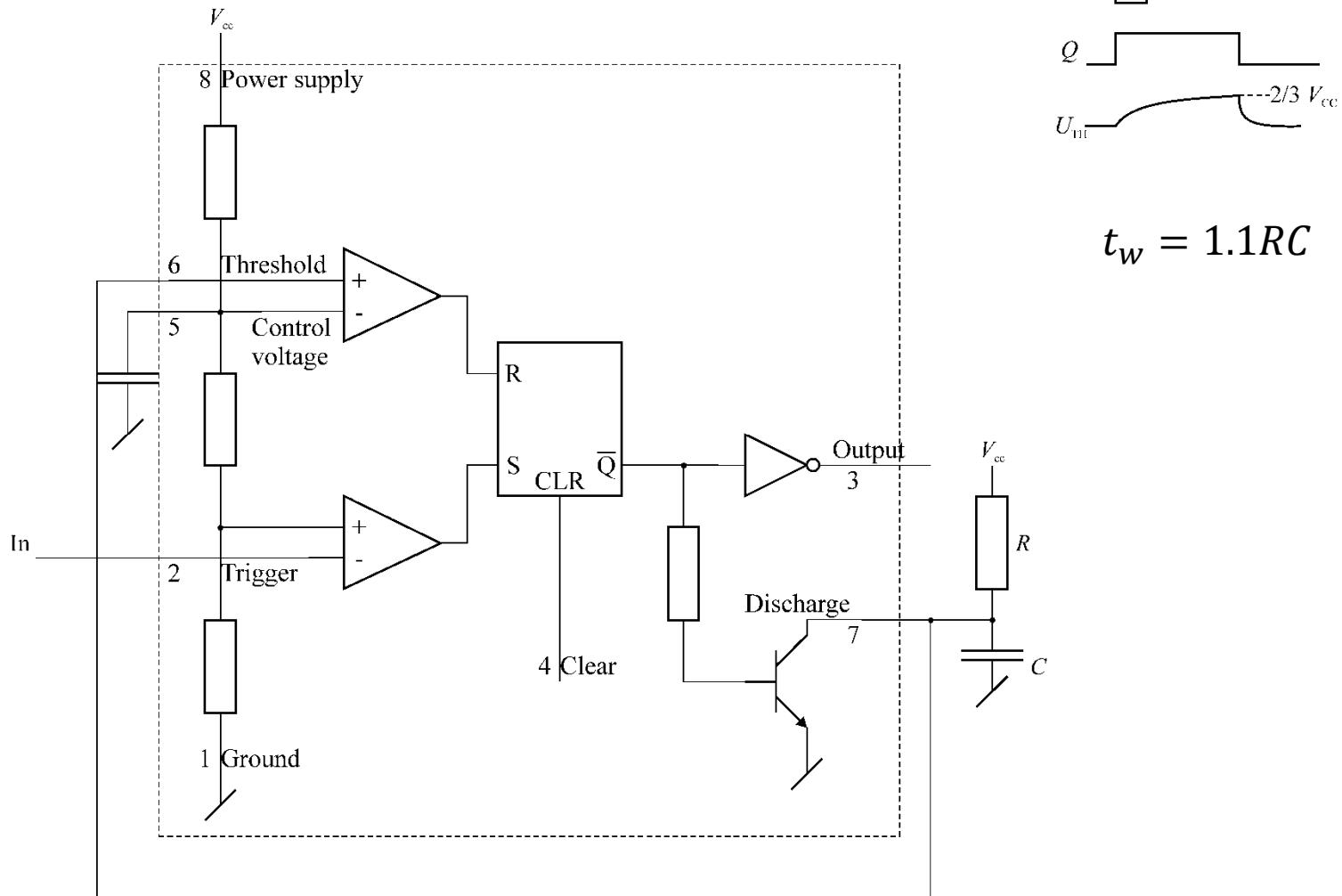

# Time circuits – part 2

- NE555 as a multivibrator (1)


$$t_{wH} = 0.693(R_A + R_B)C$$

$$t_{wL} = 0.693R_B C$$

$$f = \frac{1.44}{(R_A + 2R_B)C}$$


$$\begin{aligned}\eta &= \frac{t_{wH}}{t_{wH} + t_{wL}} = \\ &= \frac{R_A + R_B}{R_A + 2R_B} > 0.5\end{aligned}$$

$$\eta = \frac{R_B}{R_A + R_B + R_D}$$

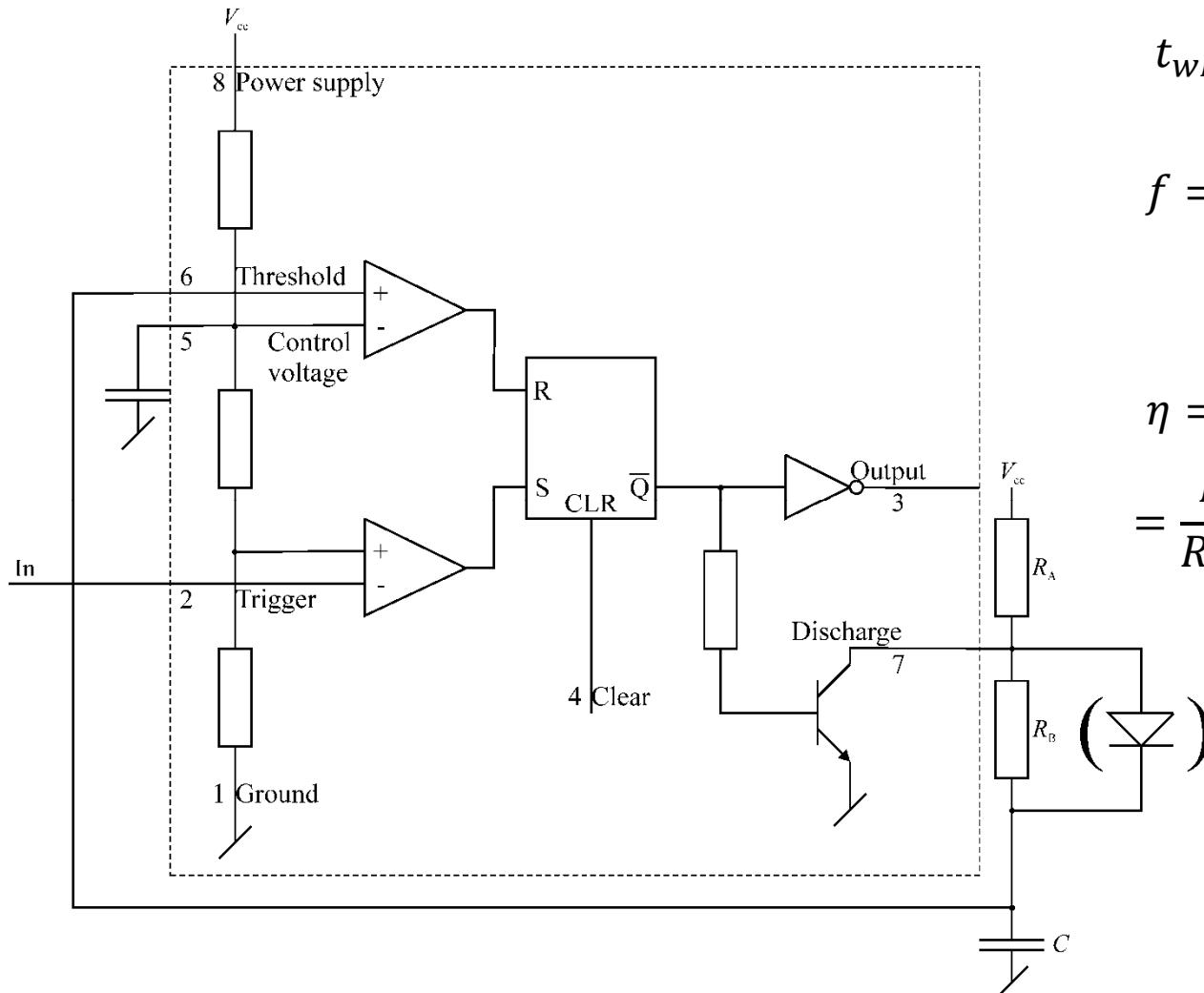


# Time circuits – part 2

- NE555 as a multivibrator (2)

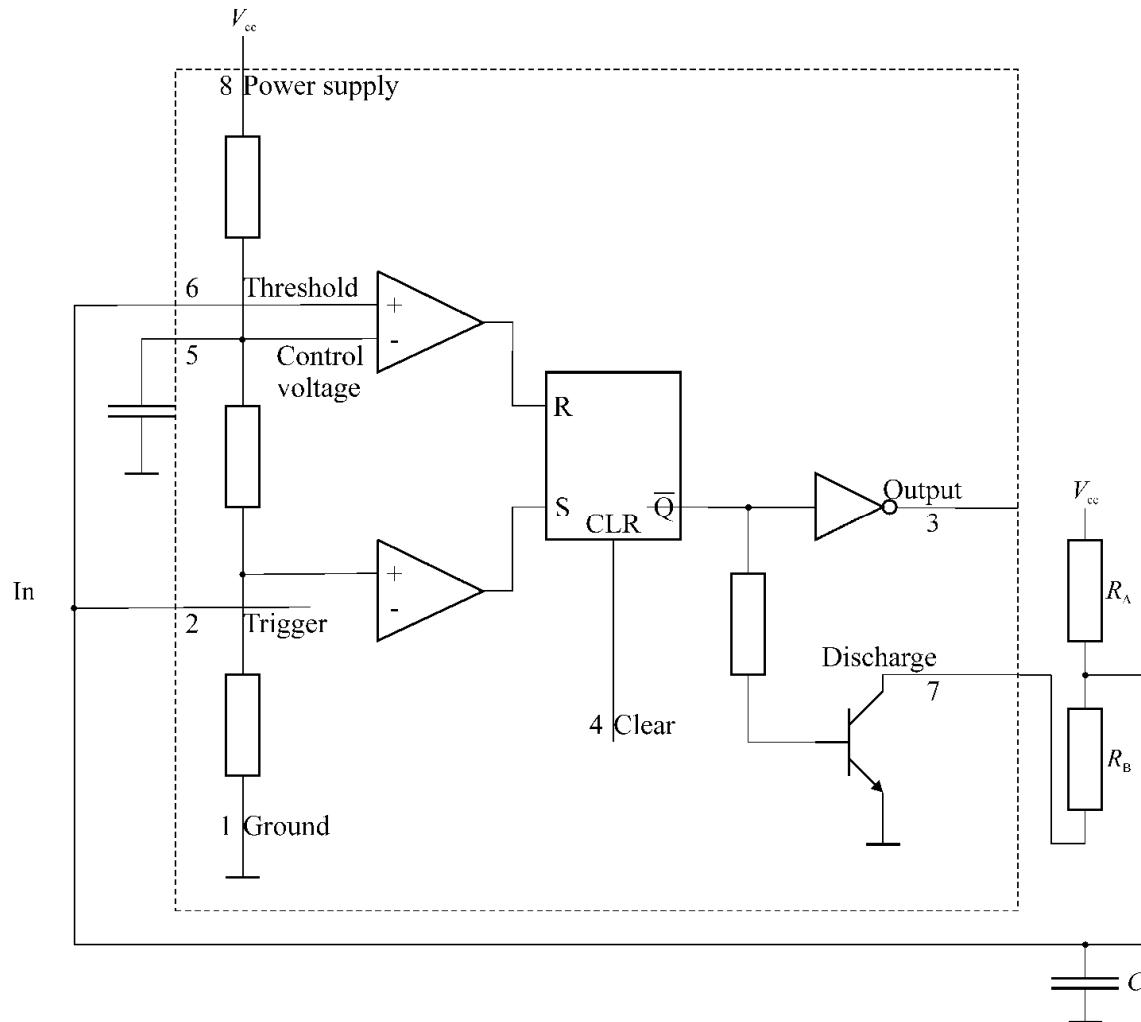

# Time circuits – part 2

- NE555 as a PWM

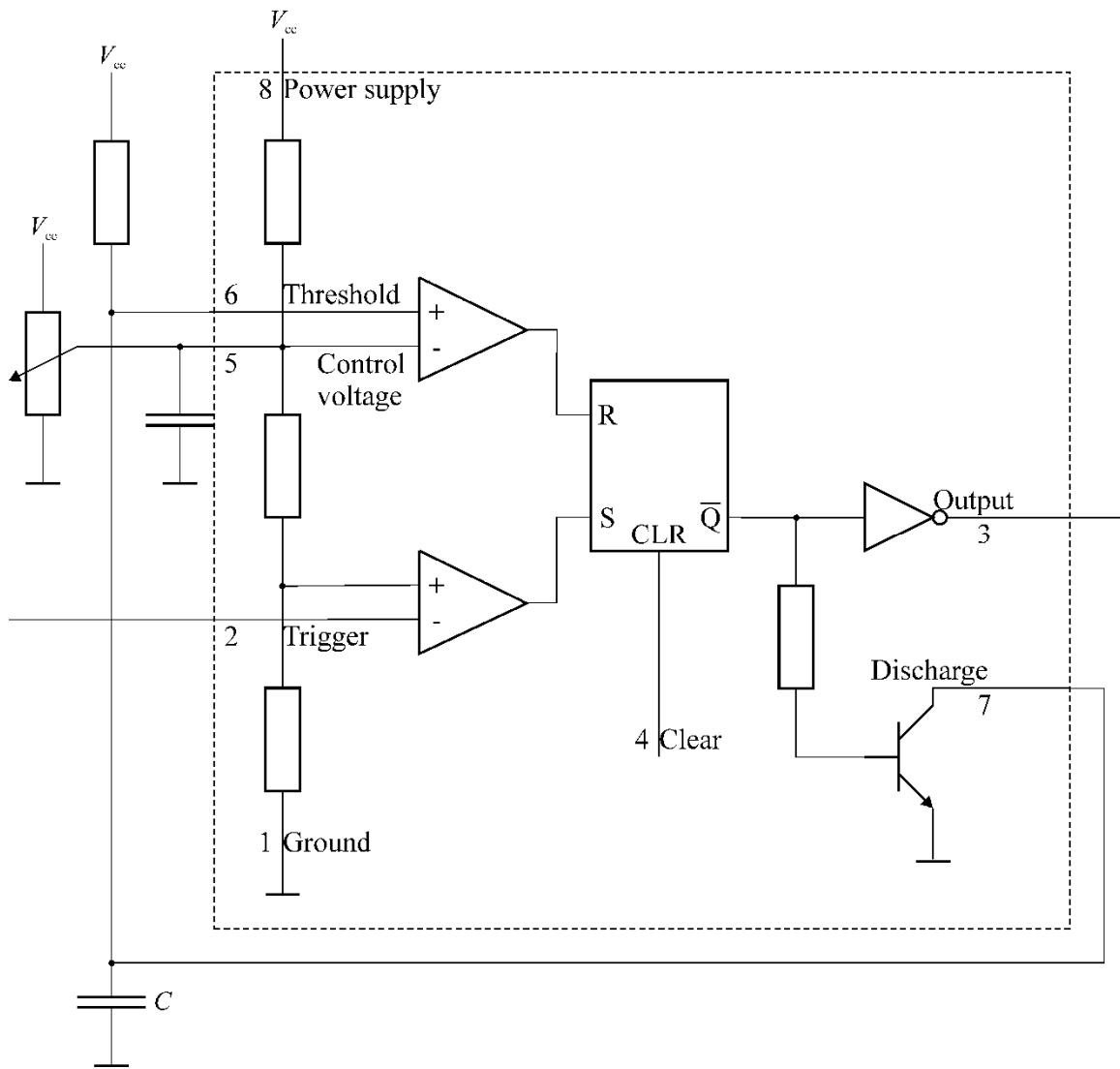


# Time circuits – part 2

- NE555 as a VCO

–  $V_5 \uparrow \rightarrow f \downarrow$

–  $R \downarrow \rightarrow f \uparrow$

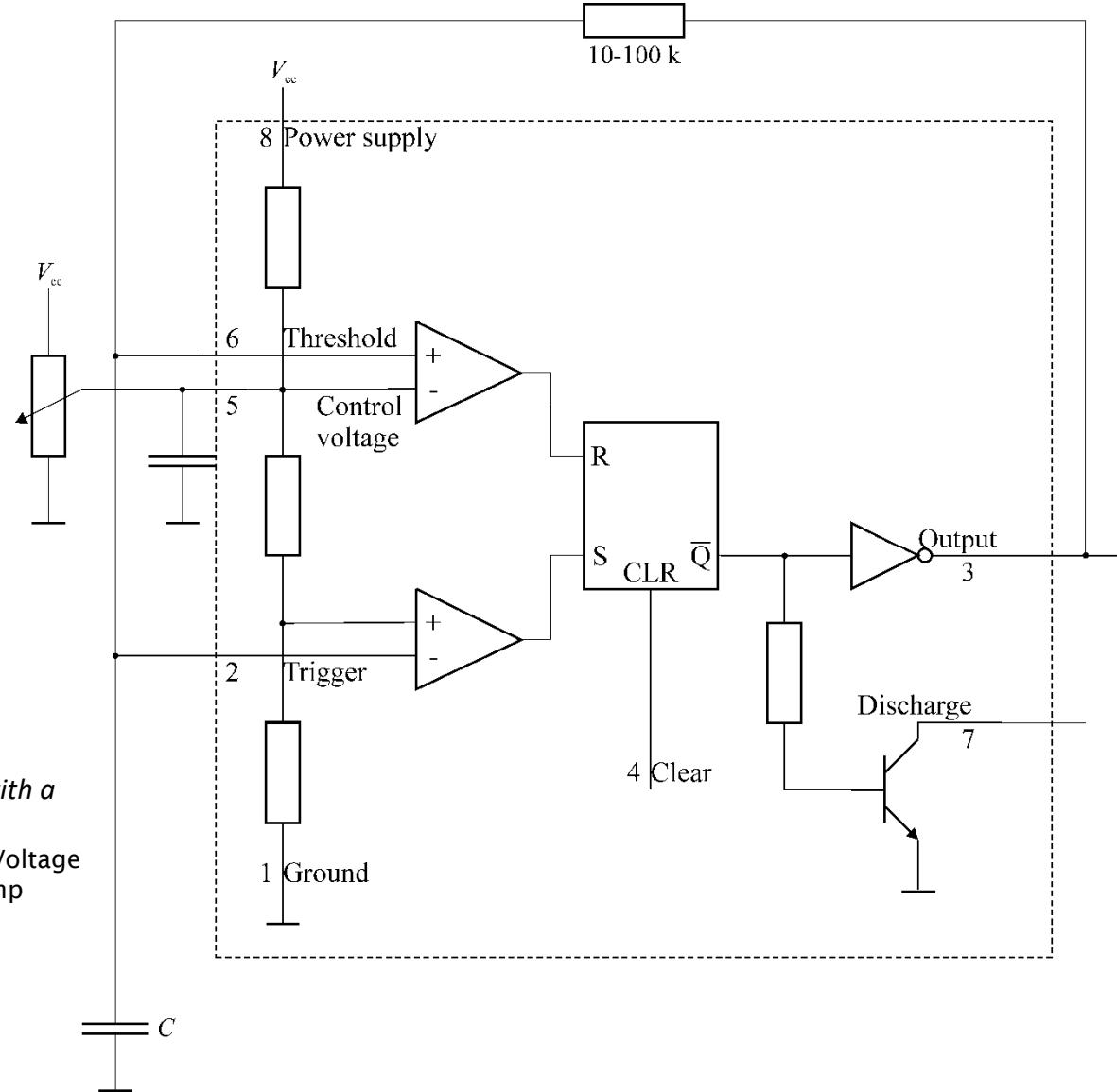

How to Build a Voltage Controlled Oscillator (VCO) with a  
555 Timer Chip  
<http://www.learningaboutelectronics.com/Articles/Voltage-controlled-oscillator-VCO-circuit-with-a-555-timer.php>


# Time circuits – part 2

---

- CMOS 4000B pulse generators
  - 4528 – double monostable multivibrator
  - 4538 – precise double monostable multivibrator
    - Both similar to 74123
    - Retriggerable
    - trigger function a little different than in 74123
  - 4047 – monostable/astable multivibrator

# Time circuits – part 2


- CMOS 4047 generator

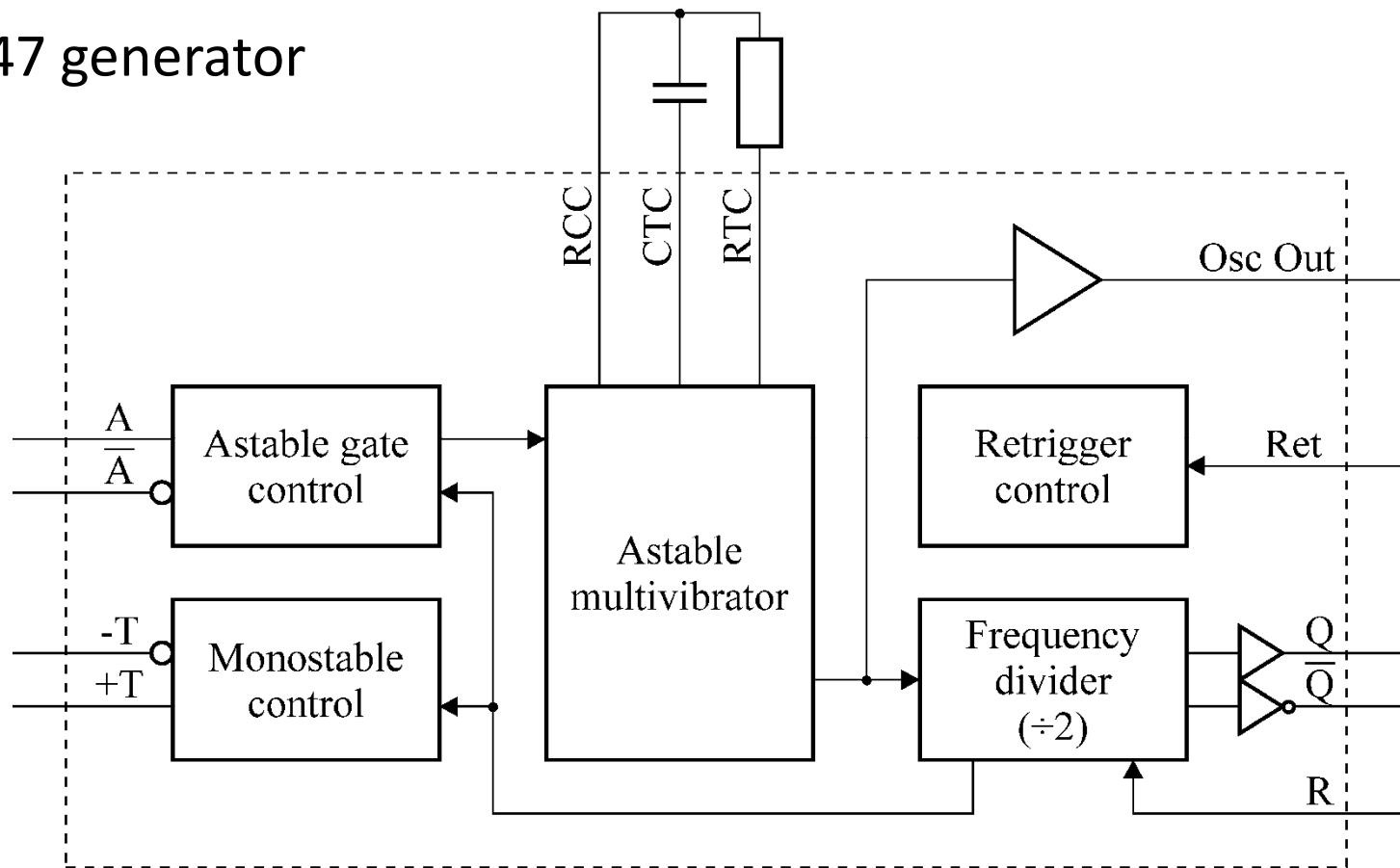

- $A(stable)$  – force astable mode
- $T(trigger)$  – force monostable mode
- $Ret(rigger), R(eset)$
- Astable mode:  $C > 100 \text{ pF}$
- Monostable mode:  $C > 1000 \text{ pF}$
- $10 \text{ k}\Omega < R < 1 \text{ M}\Omega$

# Time circuits – part 2


- 4047 as a frequency generator

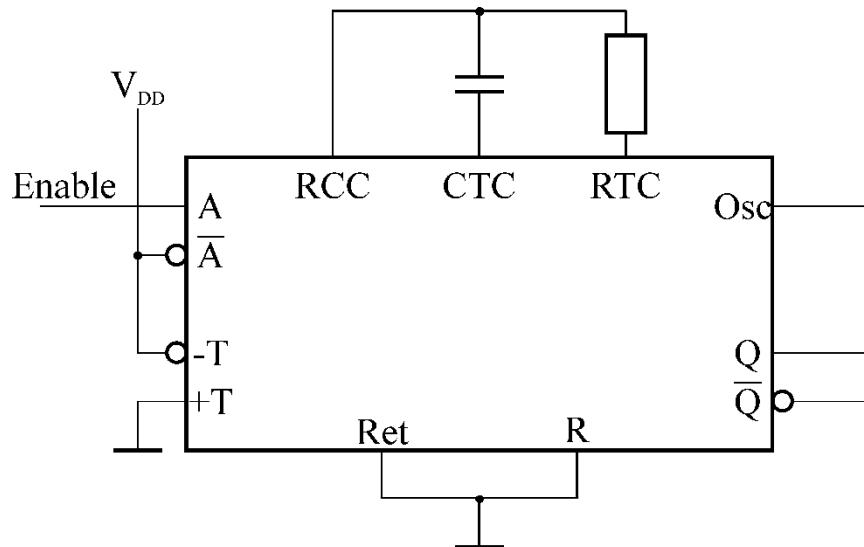

$$T_{Osc} = 2.2RC$$


$$T_Q = 4.4RC$$

$$\eta_Q = 0.5$$

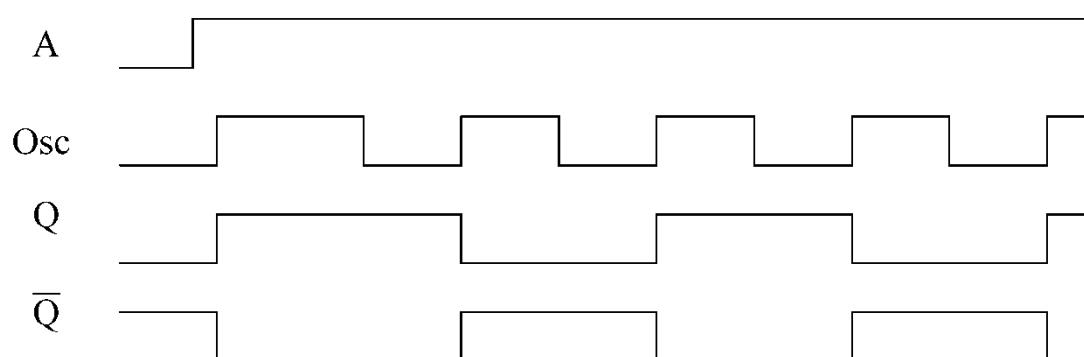

# Time circuits – part 2

- 4047 as a pulse generator

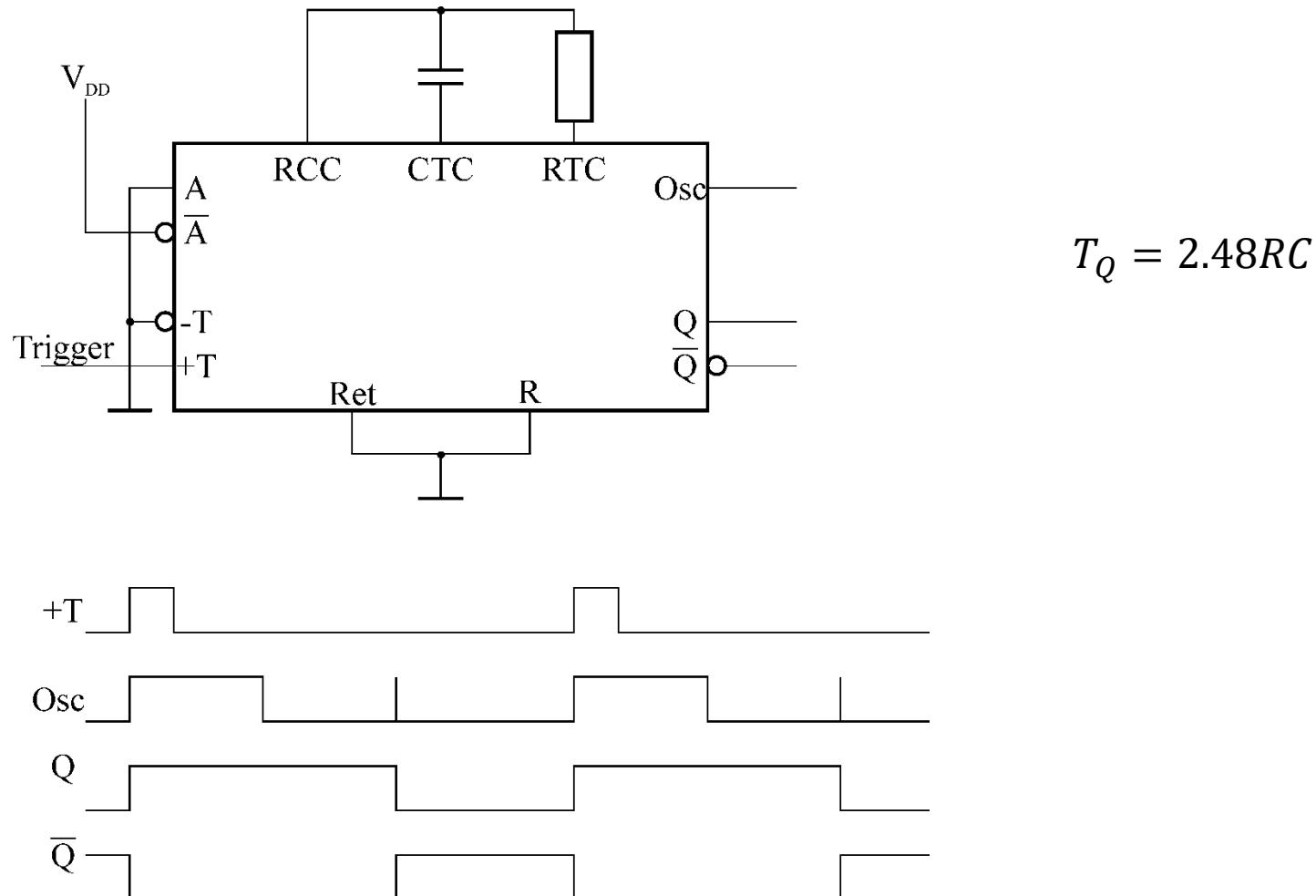

# Time circuits – part 2


---

- Trigger circuits
  - (Edge detectors, differential circuits)
    - Generate short pulses upon switch of an input signal
  - *How to do it?*
    - Integrated monostable flip-flops
    - natural gate delays
    - RC circuits

# Time circuits – part 2




---

- Trigger circuits

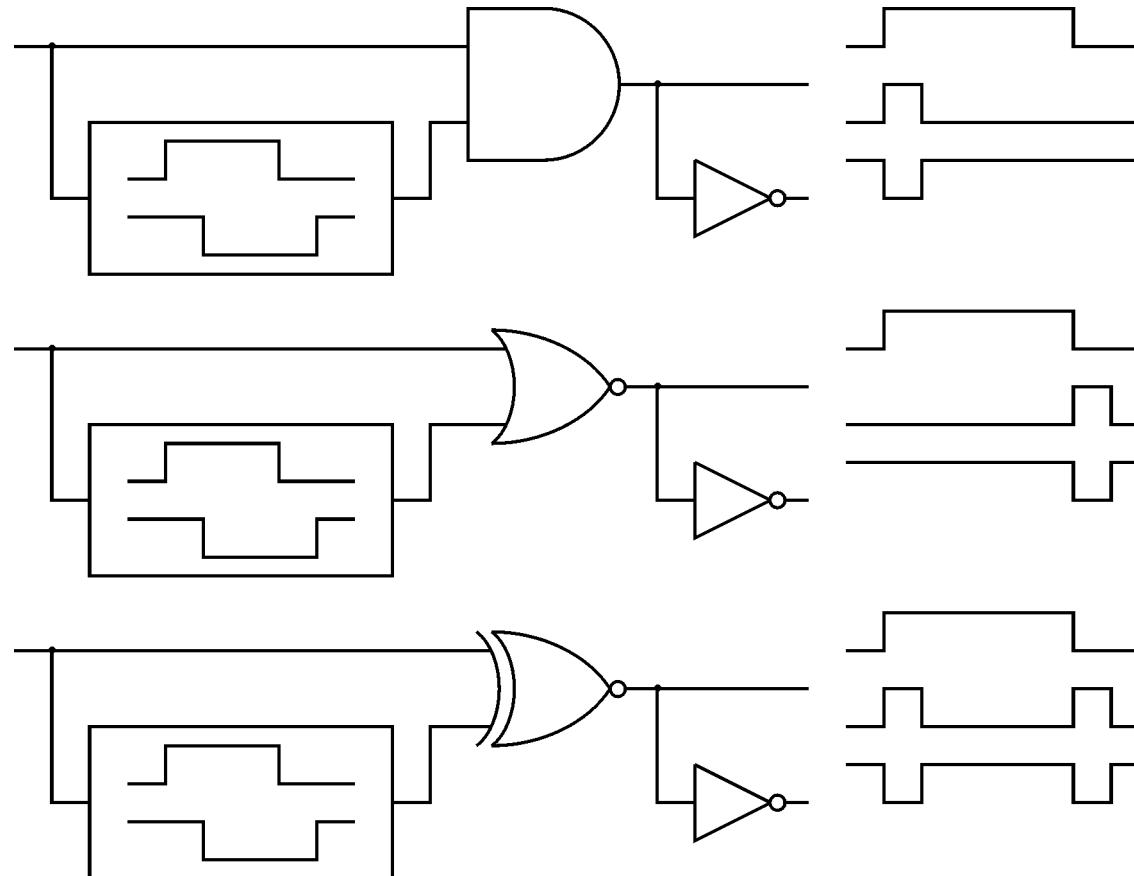


# Time circuits – part 2

---

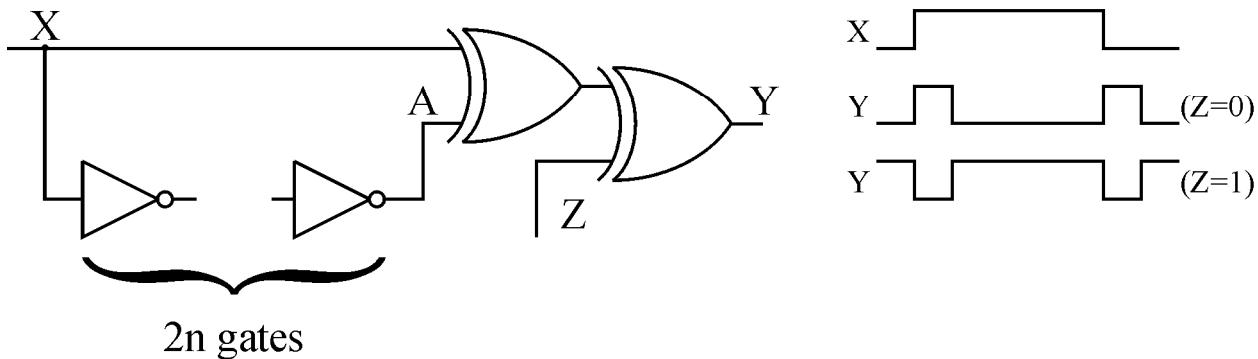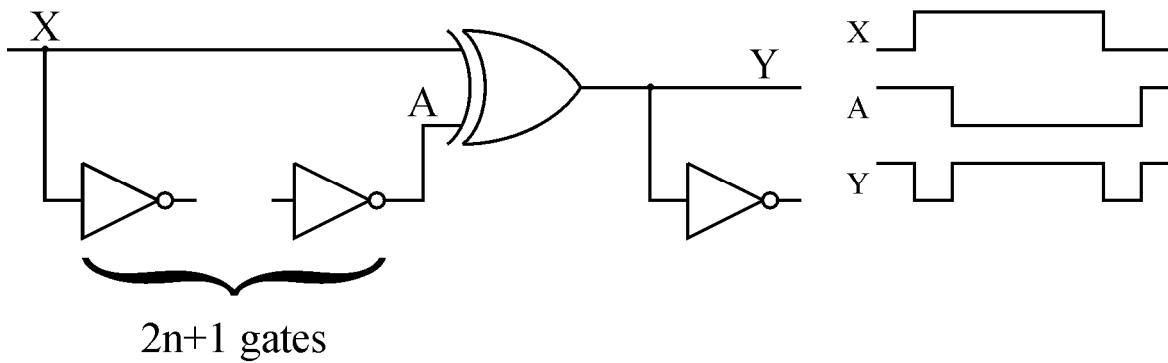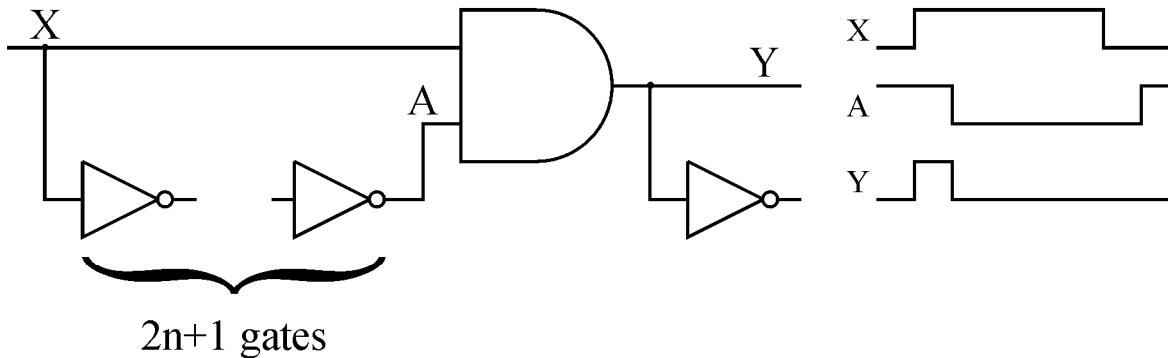


# Time circuits – part 2

---

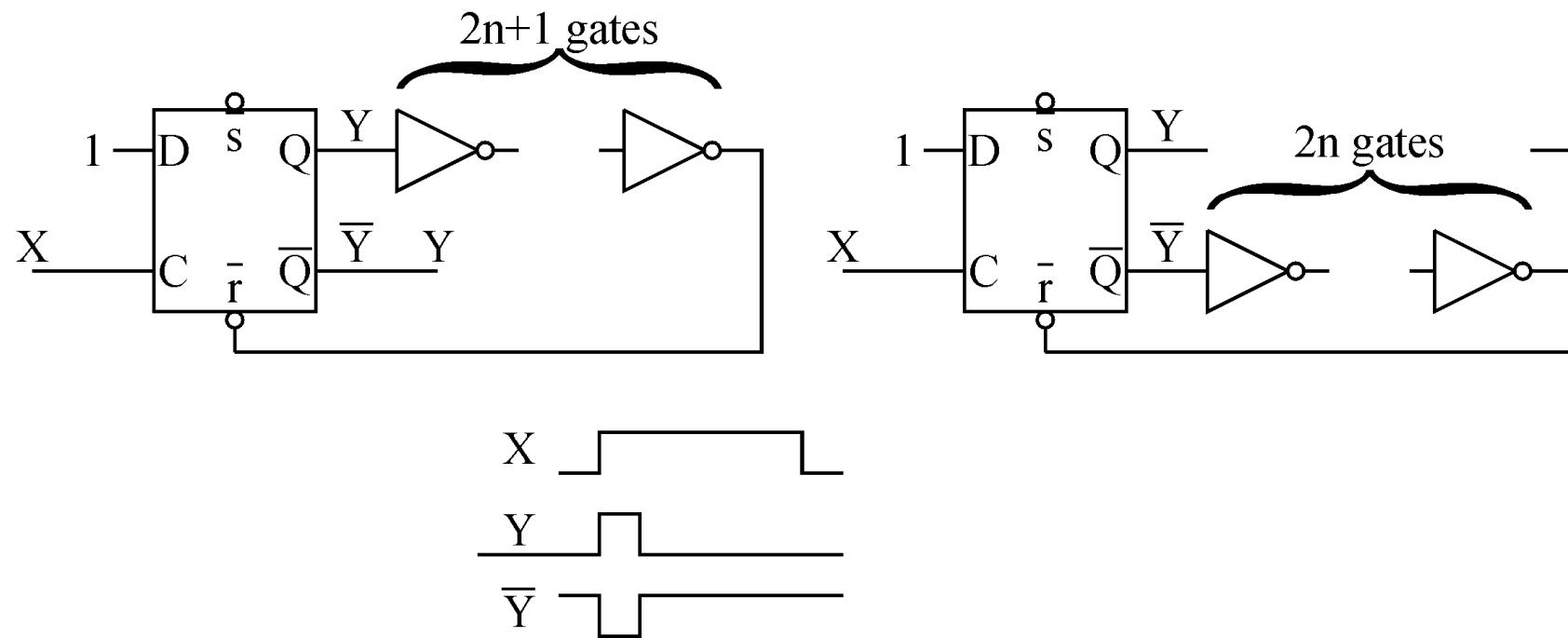

# Time circuits – part 2

---

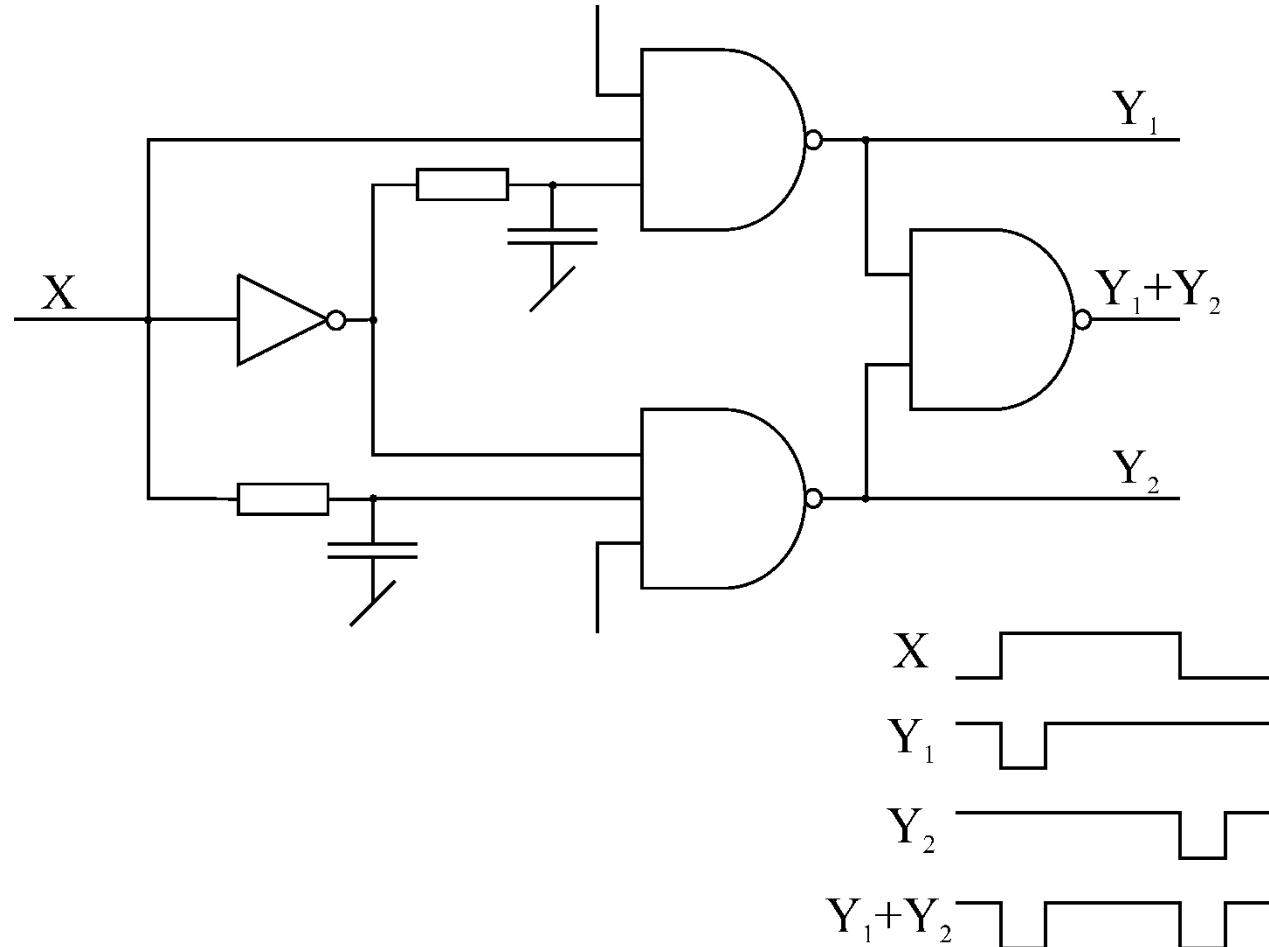

# Time circuits – part 2

---

- Frequency generators
  - parameters:
    - generated frequency stability
    - frequency range
    - duty cycle range
    - start with a non-zero phase
  - implementation:
    - 74121x, 555, etc.
    - linearised logic gates (linearised gate = linear amp.)

# Time circuits – part 2

---

- Frequency generators

