



Politechnika Śląska jako Centrum Nowoczesnego Kształcenia  
opartego o badania i innowacje


POWR-03.05.00-00-Z098/17-00

## **Digital Circuits Design**


**Faculty of Automatic Control, Electronics and Computer Science /  
Informatics, Engineer Degree, sem. 3**

# Classes 1 – Inputs and outputs of digital circuits


## Inputs and outputs

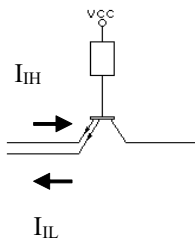

input


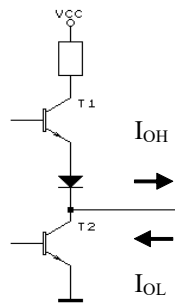


totem-pole output

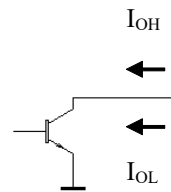


open-collector output


## Schmitt input

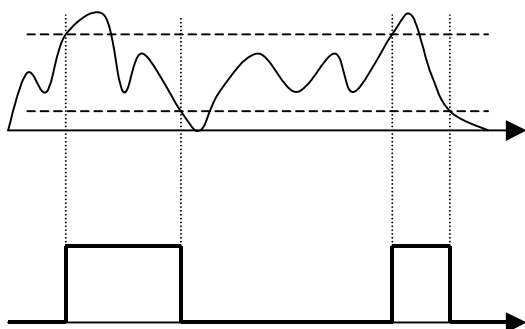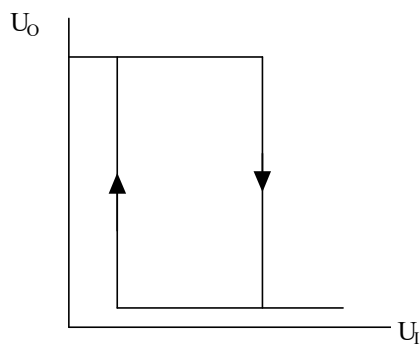
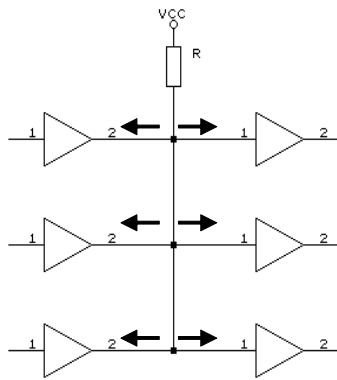
## Resistor value calculation for open-collector outputs



High state


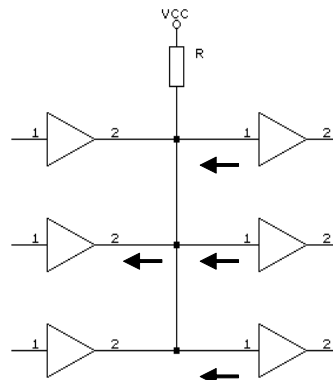


Low state


$$R_{max} = \frac{V_{CC} - \max(U_{OHmin}, U_{IHmin})}{\sum I_{OHmax} + \sum I_{IHmax}}$$

$$R_{min} = \frac{V_{CC} - \min(U_{OLmax})}{\min(I_{OLmax}) - \sum I_{ILmax}}$$

## LED connection

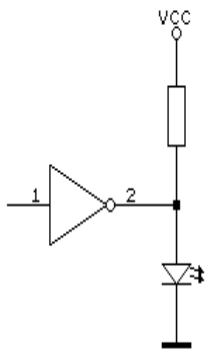
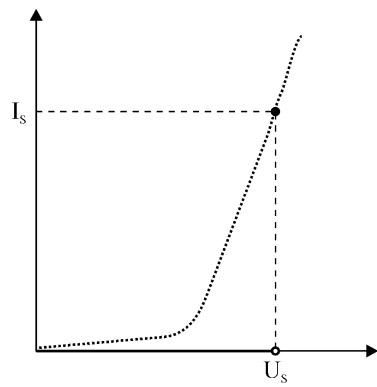

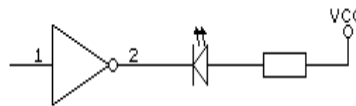
$$R_{min} = \frac{V_{CC} - U_{OLmax}}{I_{OLmax}}, \quad R_{max} = \frac{V_{CC} - U_s}{I_s}$$




$$R = \frac{V_{CC} - U_s - U_{OLmax}}{I_s}$$

**7-segment display**

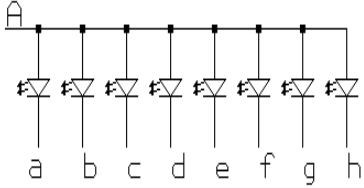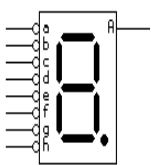

Common anode

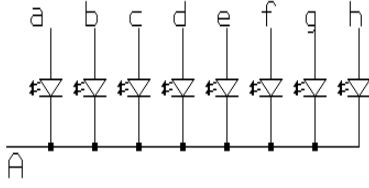

Common cathode

# Typical parameters of digital IC's


- $V_{ILmax}$  - highest input voltage in the low state
- $V_{IHmax}$  - lowest input voltage in the high state
- $V_{OLmax}$  - highest output voltage in the low state
- $V_{OHmax}$  - lowest output voltage in the high state
- $I_{ILmax}$  - highest input current in the low state
- $I_{IHmax}$  - highest input current in the high state
- $I_{OLmax}$  - highest output current in the low state
- $I_{OHmax}$  - highest output current in the high state
- $I'_{OLmax}$  - highest output current in the low state for the high-load circuits
- $I'_{OHmax}$  - highest output current in the high state for the OC outputs

Series		$V_{ILmax}$ [V]	$V_{IHmin}$ [V]	$I_{ILmax}$ [mA]	$I_{IHmax}$ [μA]	$V_{OLmax}$ [V]	$V_{OHmin}$ [V]	$I_{OLmax}$ [mA]	$I_{OHmax}$ [mA]	$I'_{OLmax}$ [mA]	$I'_{OHmax}$ [mA]
TTL	Std	0.8	2.0	1.6	40	0.4	2.4	16	0.8	48	0.25
	ALS			0.2	20	0.35	3.2	8	0.4	24	0,1
	AS			1.0	20	0.35	3.2	20	2.0	48	0,25
	F			1.2	40	0.35	3.4	20	2.0	48	
	H			2.0	50	0.2	3.4	20	1.0		
	L			0.18	10	0.2	3.4	4	0.2		
	LS			0.36	20	0.5	2.7	8	0.4	24	0.1
	S			2.0	50	0.5	2.7	20	1.0	48	0.25
CMOS	AC	1.5	3.5	1	1	0.1	4.9	24.0	24.0		
	ACT	0.8	2.0	1	1	0.1	4.9	24.0	24.0		
	C	1.5	3.5	5 nA	5 nA	0.5	4.5	1.75	1.75		
	HC	1.0	3.5	1	1	0.1	4.4	0.02	0.02		
	HCT	0.8	2.0	1	1	0.26	3.98	4.0	4.0		
	HCU	1.0	4.0	1	1	0.1	4.4	0.02	0.02		

## Examples
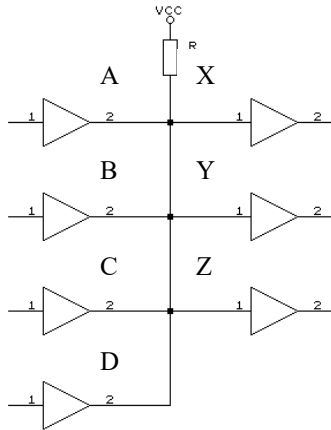
### ex. 1

For the circuit shown below calculate R so that the circuit works properly. All gates belong to the TTL series.



$$R_{max} = \frac{V_{CC} - U_{OHmin}}{N_O \cdot I_{OHmax} + N_I \cdot I_{IHmax}} = \frac{5 - 2,4[V]}{4 \cdot 250 + 3 \cdot 40[\mu A]} = \frac{2,6[V]}{1120[\mu A]} = 2321\Omega$$

$$R_{min} = \frac{V_{CC} - U_{OLmax}}{I_{OLmax} - N_I \cdot I_{ILmax}} = \frac{5 - 0,4[V]}{16 - 3 \cdot 1,6[mA]} = \frac{4,6[V]}{11,2[mA]} = 410\Omega.$$

### ex. 2

For the circuit given in the previous example calculate R. A and D gates are TTL, B – TTL LS, C – TTL S. X, Y and Z are TTL.


$$R_{min} = \frac{V_{CC} - U_{OLmaxTTL}}{I_{OLmaxLS} - N_I \cdot I_{ILmaxTTL}} = \frac{5 - 0,4[V]}{8 - 3 \cdot 1,6[mA]} = \frac{4,6[V]}{3,2[mA]} = 1438\Omega.$$

$$R_{max} = \frac{V_{CC} - U_{OHminLS}}{2 \cdot I_{OHmaxTTL} + I_{OHmaxS} + I_{OHmaxLS} + N_I \cdot I_{IHmaxTTL}} = \frac{5 - 2,7[V]}{2 \cdot 250 + 250 + 100 + 3 \cdot 40[\mu A]}$$

$$R_{max} = \frac{2,3[V]}{970[\mu A]} = 2371\Omega.$$

ex. 3

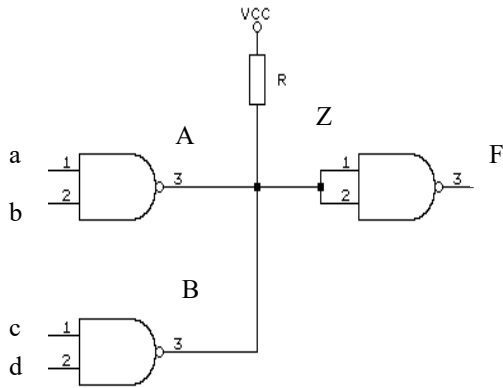For the circuit shown below calculate R so that the circuit works properly and give the logic expression describing the function implemented in the circuit. A gate is TTL, B – high power TTL (increased output load), Z – TTL S.



$$R_{max} = \frac{V_{CC} - U_{OHmin}}{N_O \cdot I_{OHmax} + I_{IHmaxS}} = \frac{5 - 2,4[V]}{2 \cdot 250 + 50[\mu A]} = \frac{2,6[V]}{550[\mu A]} = 4727\Omega,$$


$$R_{min} = \frac{V_{CC} - U_{OLmax}}{I_{OLmaxTTL} - I_{ILmaxS}} = \frac{5 - 0,5[V]}{16 - 2,0[mA]} = \frac{4,5[V]}{14[mA]} = 321\Omega.$$

$$F = \overline{\overline{(a \cdot b)} \cdot \overline{\overline{(c \cdot d)}}} = \overline{\overline{(a \cdot b)} + \overline{\overline{(c \cdot d)}}} = ab + cd.$$



ex.4

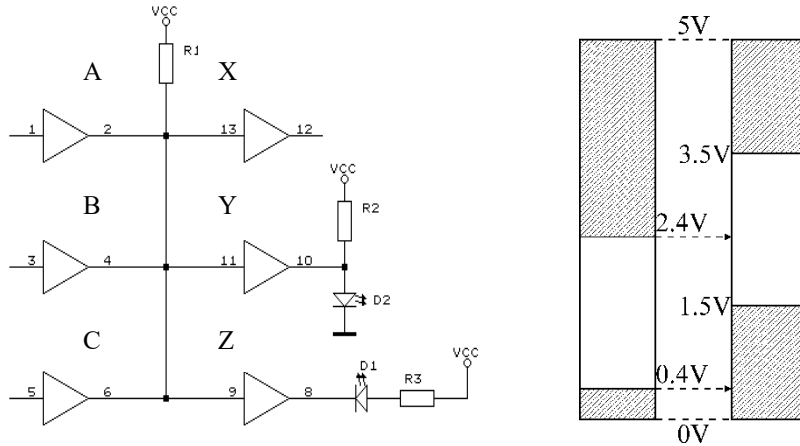For the circuit shown below calculate  $R_1$ ,  $R_2$  and  $R_3$  so that the circuit works properly. A, B and C gates belong to the TTL series. X is CMOS, Y and Z – TTL LS. Assume LED parameters:  $I_s=10\text{ mA}$ ,  $U_s=1,5\text{ V}$ .



$$R_{1max} = \frac{V_{CC} - U_{IHminCMOS}}{N_O \cdot I_{OHmaxTTL} + N_I \cdot I_{IHmaxLS}} = \frac{5 - 3,5[V]}{3 \cdot 250 + 2 \cdot 20[\mu A]} = \frac{1,5[V]}{790[\mu A]} = 1898\Omega$$

$$R_{1min} = \frac{V_{CC} - U_{OLmaxTTL}}{I_{OLmaxTTL} - N_I \cdot I_{ILmaxLS}} = \frac{5 - 0,4[V]}{16 - 2 \cdot 0,36[mA]} = \frac{4,6[V]}{15,28[mA]} = 301\Omega$$

$$R_{2max} = \frac{V_{CC} - U_s}{I_s} = \frac{5 - 1,5[V]}{10[mA]} = \frac{3,5[V]}{10[mA]} = 350\Omega$$

$$R_{2min} = \frac{V_{CC} - U_{OLmaxLS}}{I_{OLmaxLS}} = \frac{5 - 0,5[V]}{8[mA]} = \frac{4,5[V]}{8[mA]} = 562\Omega$$

$$R_3 = \frac{V_{CC} - U_s - U_{OLmaxLS}}{I_s} = \frac{5 - 1,5 - 0,5[V]}{10[mA]} = \frac{3[V]}{10[mA]} = 300\Omega$$

$R_1 = 301$  to  $1898\ \Omega$ .  $R_2$  can't be calculated, because  $R_{2max} < R_{2min}$ .  $R_3$  is not correct either, because  $I_{OL} < I_s$ .

for Y and Z gates of higher load (e.g., TTL) we get:

$$R_{2min} = \frac{V_{CC} - U_{OLmaxTTL}}{I_{OLmaxTTL}} = \frac{5 - 0,4[V]}{16[mA]} = \frac{4,6[V]}{16[mA]} = 287\Omega,$$

while  $R_3$  remains the same, but in this case it's correct.

ex.5

CMOS powered from  $V_{DD} > V_{CC}$

