



Politechnika Śląska jako Centrum Nowoczesnego Kształcenia
opartego o badania i innowacje


POWR-03.05.00-00-Z098/17-00

Digital Circuits Design

**Faculty of Automatic Control, Electronics and Computer Science /
Informatics, Engineer Degree, sem. 3**


Classes 2 – Display circuits

7-segment display controllers



 


Digit comparators

4-bit comparator

 

8-bit comparators

   


Properties of 8-bit comparators

Curcuit	gate inputs	output type	numer outputs	of pull-up resistors	Schmitt inputs
74682	-	totem-pole	2	yes	yes
74683	-	open collector	2	yes	yes
74684	-	totem-pole	2	-	yes
74685	-	open collector	2	-	yes
74686	2	totem-pole	2	-	yes
74687	2	open collector	2	-	yes
74688	1	totem-pole	1	-	-
74689	1	open collector	1	-	-




comparator outputs states

relations	$\overline{P = Q}$ output	$\overline{P > Q}$ output
$P < Q$	„1”	„1”
$P = Q$	„0”	„1”
$P > Q$	„1”	„0”

Multiplexers

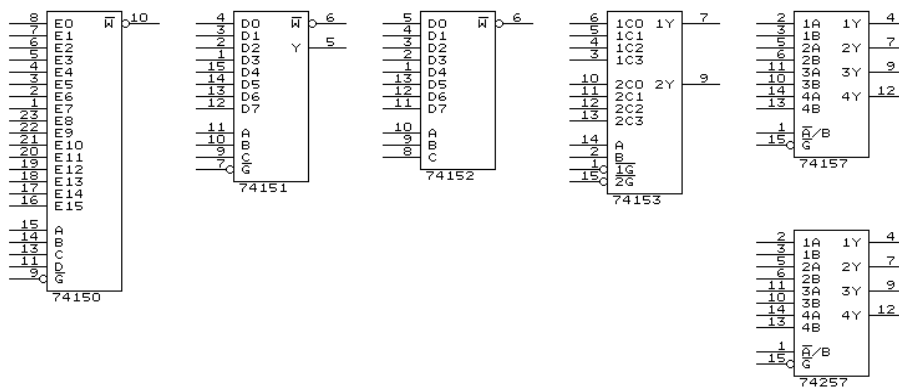


Demultiplexers

   


Time circuits

74121

$$t_w = C_T \cdot R_T \cdot \ln 2.$$

 


pins

 

trigger function

delay time determination


 


74123



$$t_w[\text{ns}] = a \cdot C_T[\text{pF}] \cdot R_T[\text{k}\Omega] \cdot \left(1 + \frac{0,7}{R_T[\text{k}\Omega]} \right).$$

$a=0,32$, $R_T=5-50 \text{ k}\Omega$, $C_T \geq 1000 \text{ pF}$; if diode is connected $a=0,28$, $R_T < 30 \text{ k}\Omega$.


pins

  



delay time determination

  

NE555

 


Pin number	Function
1	ground
2	trigger voltage
3	output
4	reset/clear (active low)
5	control voltage
6	threshold

  

Examples





Ex. 1

Design a circuit that displays two-digit decimal number. Digits are encoded in BCD 8421 code. If the number exceeds some limit, the display should pulse with few Hz frequency. Non-significant zeroes should be blanked.

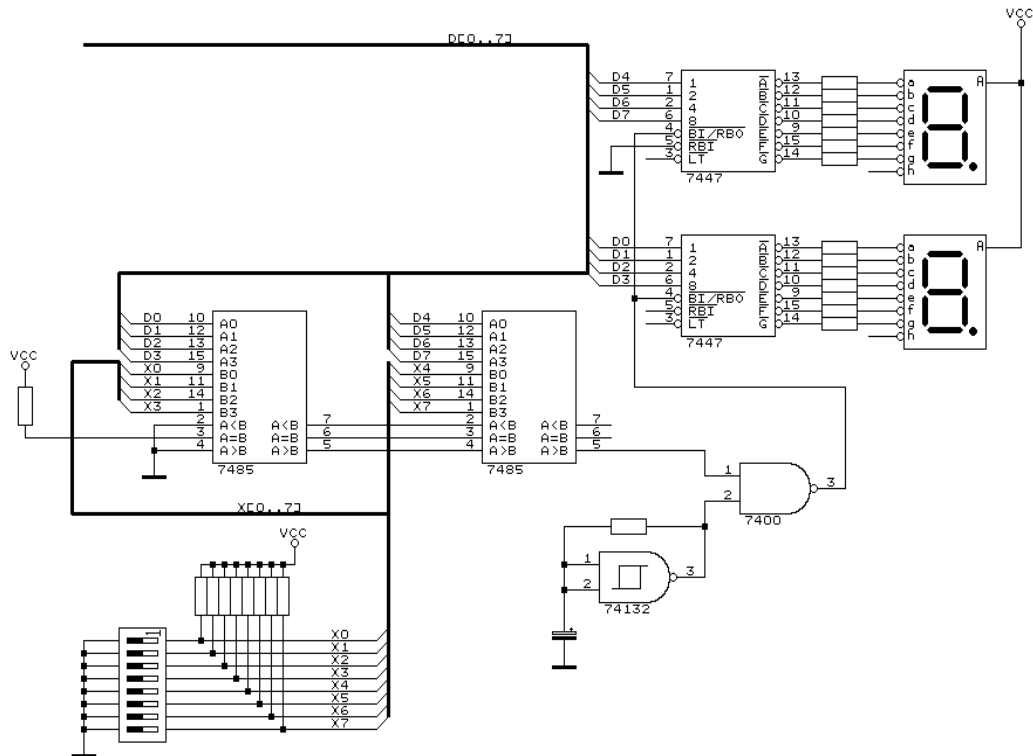

Ex. 2

Desing a „logic pen”. The information should be displayed as shown below.

  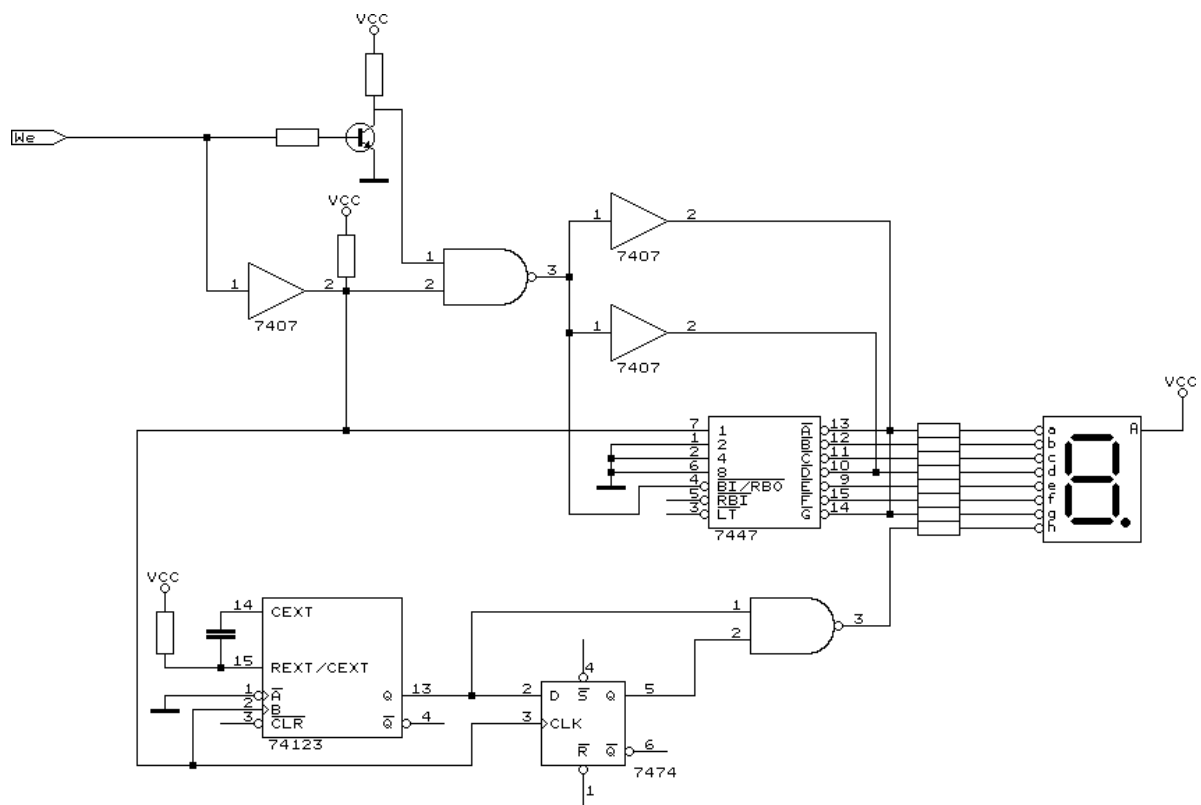 

Ex. 3

Designing a frequency generator using a single '121 circuit.

Ex. 4

Designing a 2-phase frequency generator using two '123 circuits: a) gated at the beginning of period, b) gated at the beginning of each phase.

Ex. 5

Designing a short pulse sequence generator using a single '123 circuit.

Ex. 6

Designing a frequency generator using short pulse sequence generator.

