



**Fundusze Europejskie**  
Wiedza Edukacja Rozwój



**Rzeczpospolita  
Polska**

**Unia Europejska**  
Europejski Fundusz Społeczny



**Politechnika Śląska jako Centrum Nowoczesnego Kształcenia  
opartego o badania i innowacje**

**POWR.03.05.00-IP.08-00-PZ1/17**

**Projekt współfinansowany przez Unię Europejską ze środków Europejskiego Funduszu Społecznego**

# **Microprocessor and Embedded Systems**

**Faculty of Automatic Control, Electronics and Computer Science,  
Informatics, Bachelor Degree**

# Lecture 6

---

**Serial input/output circuits**  
**Programmable timers/counters**

**Bartłomiej Zieliński, PhD, DSc**

# Serial IO/Timers

---

## Program:

- Serial IO circuits
  - Intel 8251
  - Zilog Z80 SIO (brief)
- Timers/counters
  - Intel 8253
  - Zilog Z80 CTC


# Serial IO

---

- Intel 8251 circuit
  - Programmable serial IO circuit
  - USART (**U**niversal **S**ynchronous/**A**synchronous **R**eceiver/**T**ransmitter)
  - Asynchronous
    - RS-232 compatible character format
    - Modem control
    - No built-in timer for transmission rate setting
  - Synchronous
    - Programmable synchronisation word(s)

# Serial IO

- Intel 8251 circuit pins

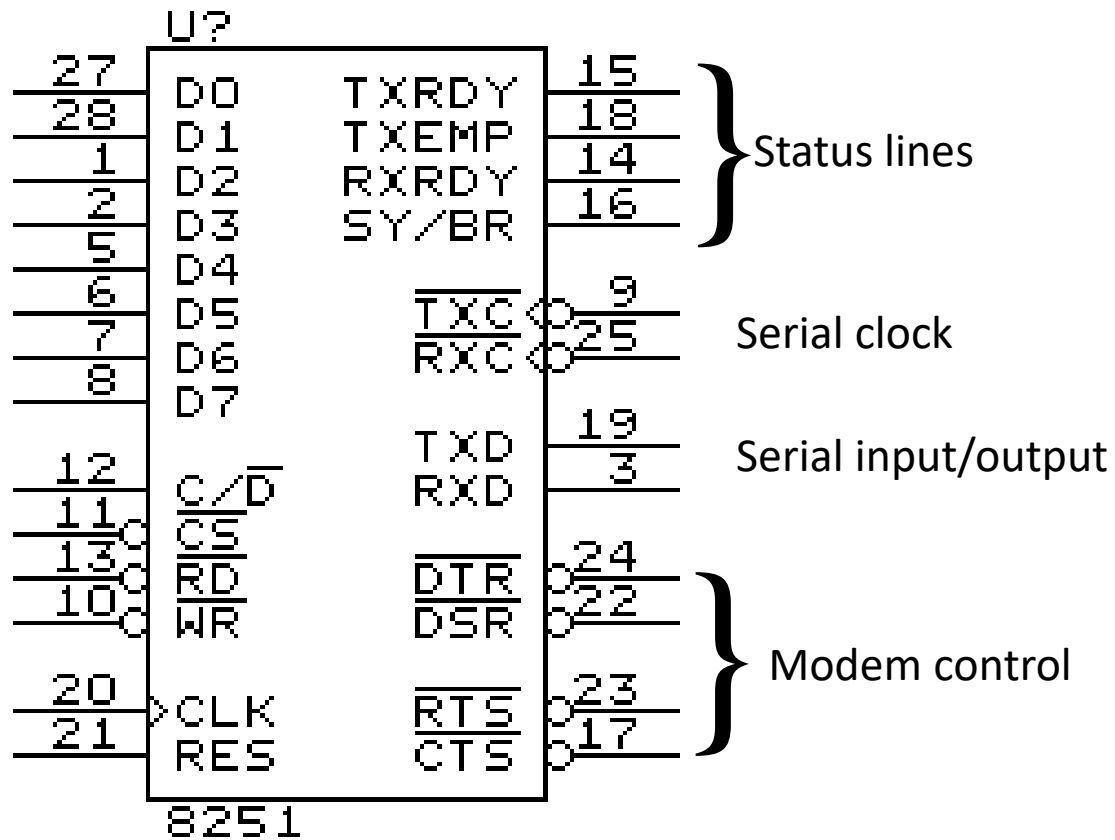

# Serial IO

---

- Serial IO + clock
  - Separate I/O signals
  - Separate clock
    - Different Tx/Rx transmission rates
  - Signals:
    - TxD (*Transmitter Data*) →
    - RxD (*Receiver Data*) ←
    - TxC (*Transmitter Clock*) ←
    - RxC (*Receiver Clock*) ←

# Serial IO

---

- Modem control
  - Comes from RS-232 standard
    - DTE (*Data Terminal Equipment*)
      - eg., computer, controller, etc.
    - DCE (*Data Communications Equipment*)
      - eg., modem, network card, etc.
  - Signals
    - DTR (*Data Terminal Ready*) →
    - DSR (*Data Set Ready*) ←
    - RTS (*Ready To Send*) →
    - CTS (*Clear To Send*) ←

# Serial IO

---

- Status

- Hardware signals

- RxRDY (*Receiver Ready*) →

- TxRDY (*Transmitter Ready*) →

- TxEMPTY (*Transmitter Empty*) →

- SynDet/BrkDet ↔

- Synchronous transmission: *Synchronisation Detected*

- » Input or output

- Asynchronous transmission: *Break Detected*


- Software status register read



# Serial IO


---

- Transmission model

 

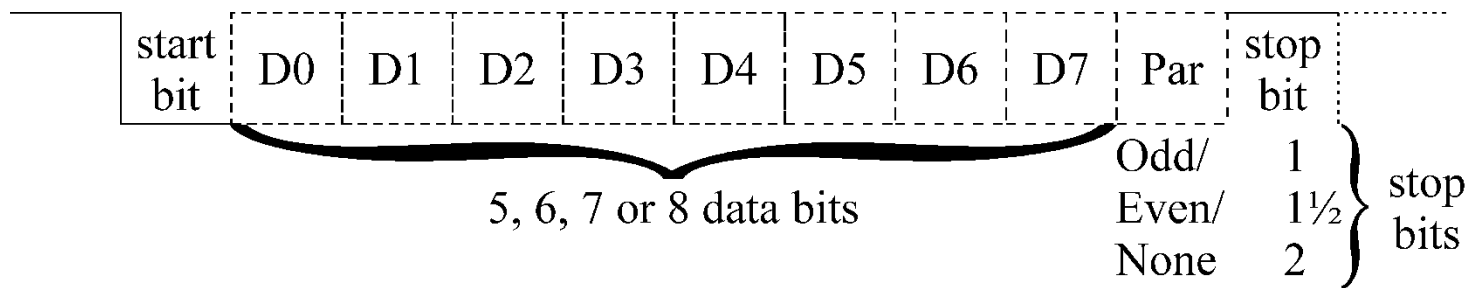
# Serial IO

- Asynchronous transmission
  - Character format




- Break condition & signalling

 

 
# Serial IO

- Synchronous transmission
  - Character format




- Information format

 

# Serial IO

---

- Programming
  - Mode word

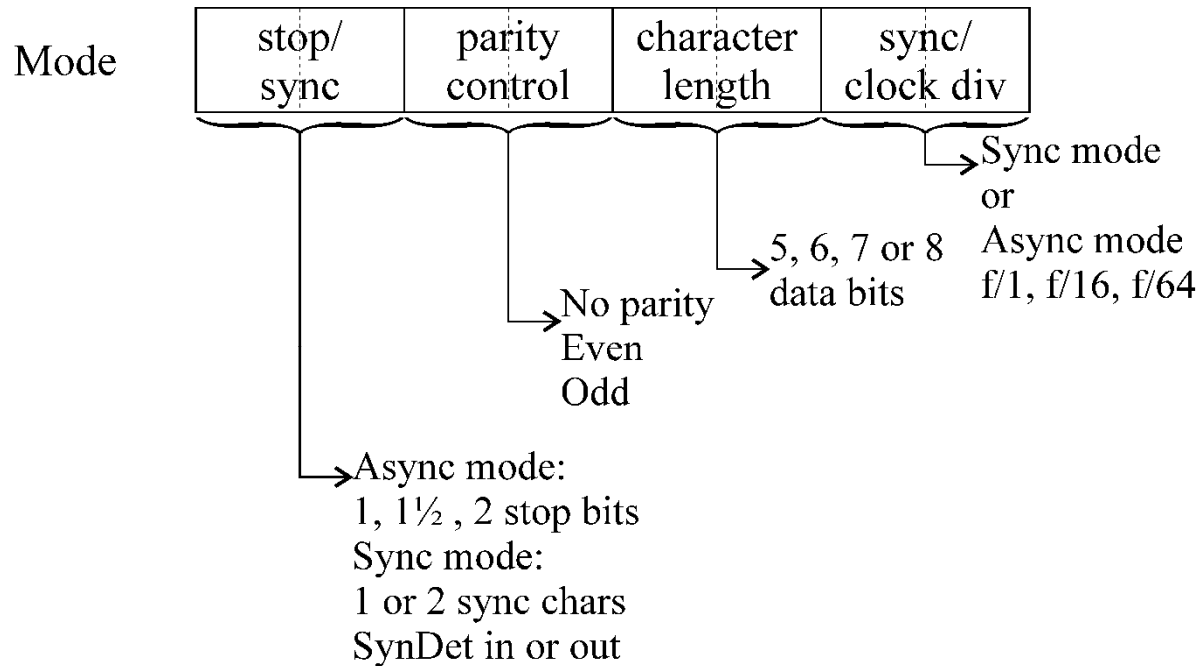


- If Sync mode selected, after Mode word, 1-2 Sync bytes

# Serial IO

---


- Programming
  - Control word

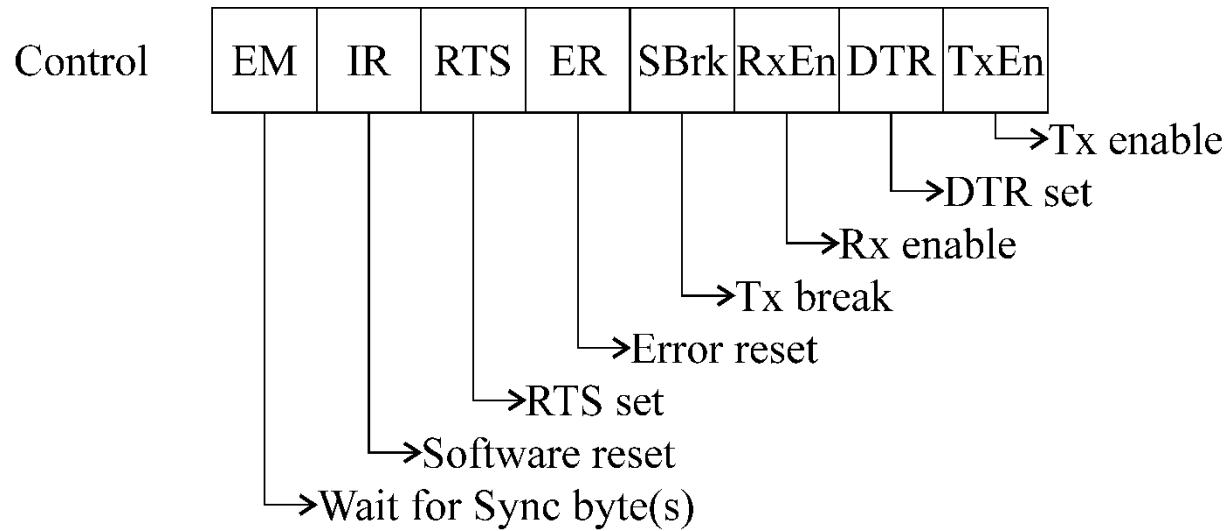

# Serial IO

---

- Programming
  - Status word

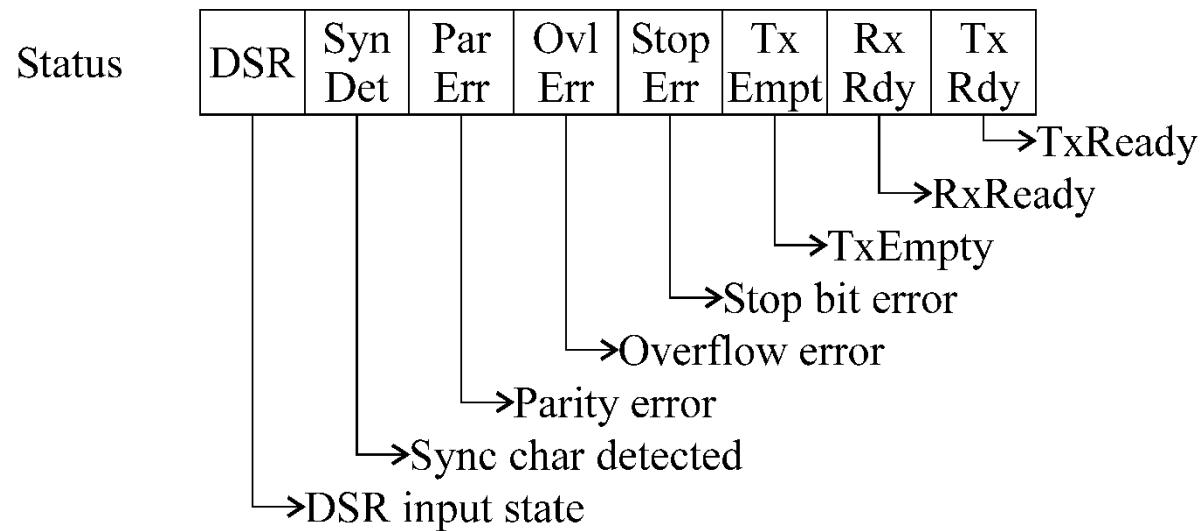

# Serial IO

---

- Other serial transmission IC's
  - Z80 SIO (*Serial Input/Output*)
    - 2 serial syn/asyn serial ports
      - Asyn: RS-232 compatible
      - Syn: IBM Bisync, SDLC, HDLC, AX.25 protocols
        - » Automatic CRC calculation, transmission and check
        - » Automatic sync character insertion and removal
        - » Bit stuffing
  - 8530/82530
    - Z80 SIO for  $\mu$ p others than Z80
  - 8250/16450/16550...16950
    - Single serial port for PC-class computers

# Timers/counters

---


- Intel 8253
  - 3 independent, 16-bit counters
  - Binary/decimal counting
  - Count from initial value to 0
  - 6 modes
  - Mode-dependent Gate input
    - gate, trigger, clear



# Timers/counters

---


- Intel 8253 circuit pins

 
 
# Timers/counters

---


- Intel 8253 modes
  - Mode 0: „counter”
    - Mode write: Out=0
    - Gate=0: disable count
    - Counted to 0: Out=1 and stop


 
# Timers/counters

---


- Intel 8253 modes
  - Mode 1: „one shot (univibrator)” (retriggerable)
    - Gate 0→1: count start, Out=0
    - Gate 0→1 during count: count restart
    - Counted to 0: Out=1


 
# Timers/counters

---


- Intel 8253 modes
  - Mode 2: „rate generator” (divide-by-N counter)
    - Initially Out=1
    - Counted to 1: Out=0 for 1  $T_{clk}$  and continue
    - Gate=1: enable; Gate=0: disable counting


 
# Timers/counters

---


- Intel 8253 modes
  - Mode 3: „square wave generator”
    - Gate 0→1: start counting (e.g., for synchronisation)
    - Counted to 0:  $Out = \overline{Out}$
    - For each  $N$ ,  $T_{Out} = N \cdot T_{Clk}$


 
# Timers/counters

---


- Intel 8253 modes
  - Mode 4: „software triggered strobe”
    - Gate=1: count starts after initial value is written
    - Gate=0: count stops
    - Gate 0→1: count reset


 
# Timers/counters

---

- Intel 8253 modes
  - Mode 4: „hardware triggered strobe”
    - Gate=0→1: count starts
    - Gate=0: count continues
    - Gate 0→1: count reset



# Timers/counters

---

- Intel 8253 – Gate operation summary

| Mode | 0, 1→0                 | 0→1                            | 1            |
|------|------------------------|--------------------------------|--------------|
| 0    | Disable count          |                                | Enable count |
| 1    |                        | Initiate count<br>Reset output |              |
| 2    | Disable count<br>Out=1 | Reinitiate<br>count            | Enable count |
| 3    | Disable count<br>Out=1 | Reinitiate<br>count            | Enable count |
| 4    | Disable count          |                                | Enable count |
| 5    |                        | Initiate count                 |              |




# Timers/counters

- Intel 8253 programming

| $A_1A_0$ | 00      | 01      | 10      | 11      |
|----------|---------|---------|---------|---------|
| Register | T0 data | T1 data | T2 data | Control |

## – Mode/control register

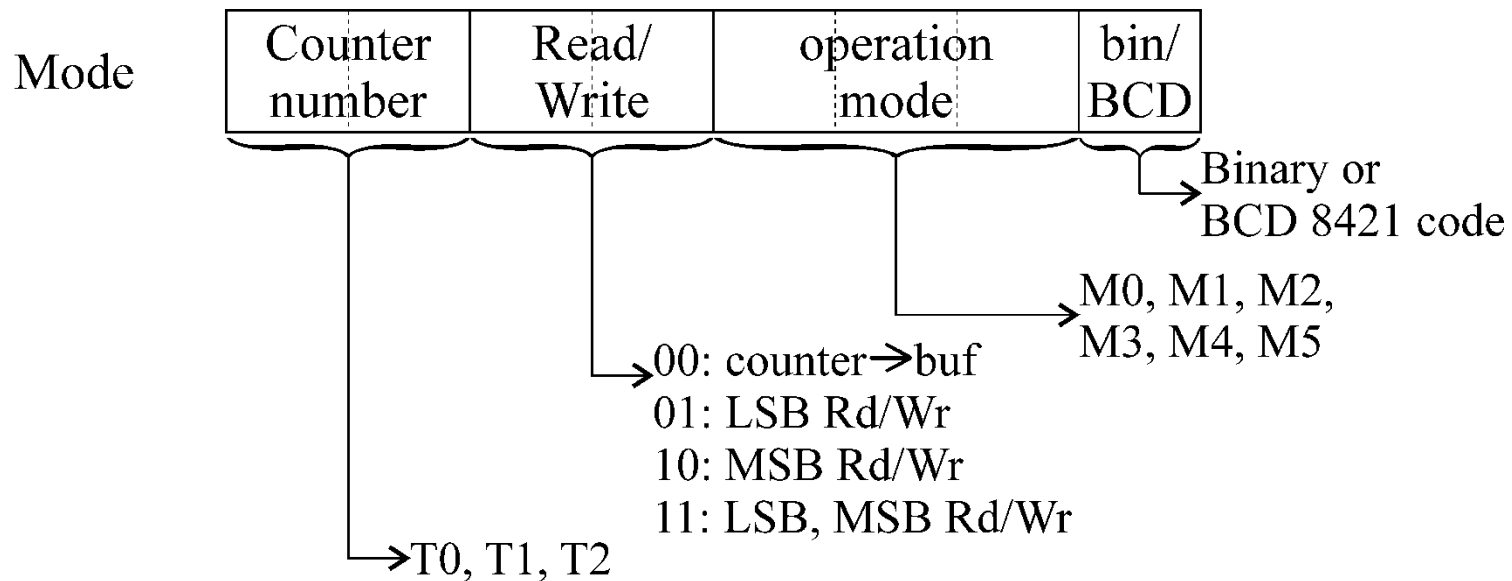

# Timers/counters

---

- Intel 8254 programming extensions
  - „Read-back” command
    - Read counter content
    - Read counter mode
    - Store counter content in a register
      - Counters bit-map selectable
  - Status command
    - Out pin status
    - Counter can be read
    - Counter mode / code

# Timers/counters


---

- Zilog Z80 CTC
  - 4 independent, 8-bit counters
  - Timer/counter operation
  - Count from initial value to 0
    - Automatic hardware reload
  - Counting start can be triggered
  - Out signal (for 3 counters only)
  - Interrupt generation
    - Can work as an interrupt controller for non-Z80 family circuits (e.g., 8255, 8253.....)

# Timers/counters

---


- Zilog Z80 CTC circuit pins

 
 
# Timers/counters

---


- Zilog Z80 CTC modes
  - Counter mode
    - Clk/Trg = input (active value software selectable)
    - Counted to 0: Out pulse
    - Can generate interrupt



# Timers/counters

---


- Zilog Z80 CTC modes
  - Timer mode
    - Clk/Trg = optional counting start
    - Counted to 0: Out pulses,  $\eta=1/2$ ,  $T=T_{\text{clk}} * [16 | 256] * T_c$
    - Can generate interrupt

 
 
# Timers/counters

---


- Zilog Z80 CTC programming
  - Interrupt vector
    - Common (software definable) part
    - Timer number (automatically generated) part
    - One word for all counters



- Mode/control word
  - For each timer separately
  - Time constant must be announced
  - Timer read any time
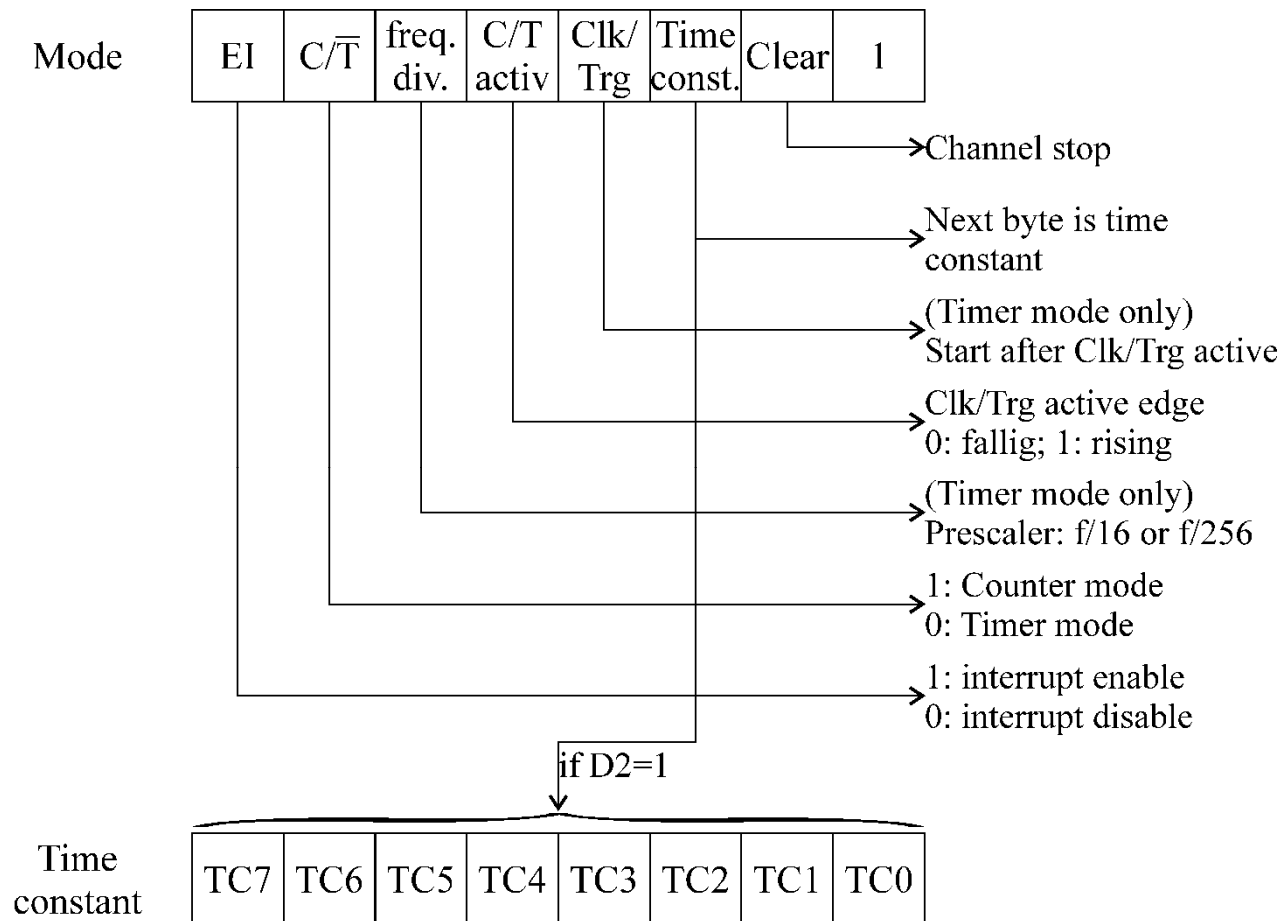
# Timers/counters


- Zilog Z80 CTC programming
  - Mode/control




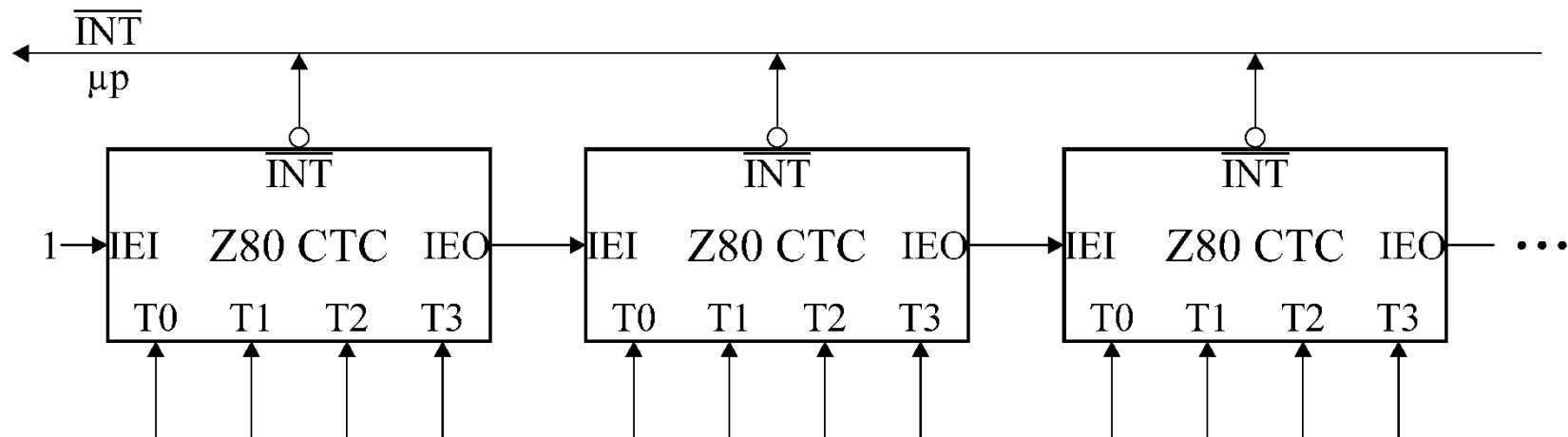
# Timers/counters

- Zilog Z80 CTC interrupts
  - T0 – highest priority, T3 – lowest priority
  - Individual vectors for each counter
  - May work as an interrupt controller for non-Z80 family IC's
  - „distributed interrupt controller” concept



# Timers/counters

---

- Zilog Z80 CTC interrupts
  - For „external” interrupt inputs
    - Counter mode
    - Time constant = 1
    - Hardware time constant reload
    - Programmable active interrupt signal edge
    - Software masking
  - For other counters/timers
    - Anything we need

# Timers/counters

---

- Zilog Z80 CTC reset
  - Count operations terminate
  - All interrupts disable
  - ZC/TO and INT lines inactive
  - IEO=IEI
  - Data lines – high impedance